
Contents

<i>Foreword</i>	<i>ix</i>
<i>Preface</i>	<i>xi</i>
<i>Road Map to the Syllabus</i>	<i>xiii</i>
1. Electron Dynamics and CRO	1.1-1.38
1.1 Introduction	1.1
1.2 Charged Particles	1.2
1.3 Force, Field Intensity, Potential Energy	1.2
1.4 Two Dimensional Motion of Electron	1.5
1.5 Force in a Magnetic Field	1.10
1.6 Motion in a Magnetic Field	1.11
1.7 Parallel Electric and Magnetic Fields	1.14
1.8 Perpendicular Electric and Magnetic Fields	1.14
1.9 Electrostatic Deflection in Cathode Ray Tube	1.18
1.10 Magnetic Deflection in Cathode Ray Tube	1.22
1.11 Comparison Between Electric and Magnetic Deflection Systems	1.24
1.12 Cathode Ray Oscilloscope (CRO)	1.25
<i>Review Questions</i>	1.34
<i>Objective Type Questions</i>	1.36
2. Junction Diode Characteristics	2.1-2.79
2.1 Introduction	2.1
2.2 Classification of Semiconductors	2.1
2.3 Conductivity of Semiconductor	2.5
2.4 Energy Distribution of Electrons	2.6
2.5 Carrier Concentration in Intrinsic Semiconductor	2.8
2.6 Mass-Action Law	2.14
2.7 Properties of Intrinsic Semiconductors	2.19
2.8 Variation in Semiconductor Parameters with Temperature	2.20
2.9 Drift and Diffusion Currents	2.22
2.10 Carrier Life Time	2.24
2.11 Continuity Equation	2.26
2.12 Hall Effect	2.28
2.13 Theory of PN Junction Diode	2.31

2.14	Energy Band Structure of Open Circuited PN Junction	2.38
2.15	PN Diode Current Equation	2.41
2.16	Diode Resistance	2.45
2.17	Transition or Space Charge (or Depletion Region) Capacitance (C_T)	2.46
2.18	Diffusion (or Storage) Capacitance (C_D)	2.49
2.19	Effect of Temperature on PN Junction Diodes	2.50
2.20	Junction Diode Switching Characteristics.....	2.52
2.21	Breakdown in PN Junction Diodes	2.55
2.22	PN Diode Applications	2.56
2.23	Zener Diode	2.57
2.24	Varactor Diode	2.58
2.25	Tunnel Diode	2.59
2.26	Light Emitting Diode (LED)	2.63
2.27	Photodiode	2.65
2.28	Liquid Crystal Display (LCD)	2.67
2.29	Specifications of Semiconductor Diodes	2.71
	<i>Review Questions</i>	2.71
	<i>Objective Type Questions</i>	2.75
3.	Rectifiers, Filters and Regulators	3.1-3.42
3.1	Introduction	3.1
3.2	Linear Mode Power Supply	3.1
3.3	Rectifiers	3.3
3.4	Filters	3.15
3.5	Voltage Regulators	3.24
	<i>Review Questions</i>	3.37
	<i>Objective Type Questions</i>	3.40
4.	Transistor Characteristics	4.1-4.85
4.1	Introduction to Bipolar Junction Transistor	4.1
4.2	Construction of BJT	4.1
4.3	Transistor Biasing	4.2
4.4	Operation of NPN Transistor	4.3
4.5	Operation of PNP Transistor	4.3
4.6	Types of Transistor Amplifier Configuration.....	4.6
4.7	Breakdown in Transistors	4.15
4.8	Ebers-Moll Model	4.17
4.9	Introduction to Field Effect Transistor.....	4.25
4.10	Construction of N-channel JFET	4.25
4.11	Operation of N-channel JFET	4.26
4.12	Characteristic Parameters of the JFET	4.28
4.13	Expression for Saturation Drain Current	4.32
4.14	Slope of the Transfer Characteristic at I_{DSS}	4.33
4.15	FET Amplifiers	4.34
4.16	The FET Model at High Frequency	4.42
4.17	Frequency Response of FET Amplifier	4.48

4.18	Comparison of JFET and BJT	4.49
4.19	Applications of JFET	4.50
4.20	Metal Oxide Semiconductor Field Effect Transistor (MOSFET).....	4.50
4.21	Enhancement MOSFET	4.50
4.22	Depletion MOSFET	4.52
4.23	Comparison of MOSFET with JFET	4.53
4.24	Handling Precautions for MOSFET.....	4.54
4.25	Comparison of N- with P-channel MOSFETs	4.55
4.26	Comparison of N- with P-channel FETs.....	4.56
4.27	FET as Voltage-variable Resistor (VVR)	4.56
4.28	UJT (Unijunction Transistor)	4.57
4.29	PNPN Diode (Shockley Diode)	4.61
4.30	SCR (Silicon Controlled Rectifier)	4.62
4.31	Thyristor Ratings	4.65
4.32	Rectifier Circuits using SCR	4.65
4.33	LASCR (Light Activated SCR)	4.71
4.34	TRIAC (Triode a.c. Switch)	4.71
4.35	DIAC (Diode a.c. Switch)	4.73
4.36	Specifications of Transistors	4.74
	<i>Review Questions</i>	4.74
	<i>Objective Type Questions</i>	4.77
5.	Biassing and Stabilisation	5.1-5.31
5.1	Introduction	5.1
5.2	Bias Stability	5.1
5.3	Methods of Transistor Biassing	5.7
5.4	Bias Compensation	5.21
5.5	Thermal Runaway and Thermal Stability	5.22
	<i>Review Questions</i>	5.27
	<i>Objective Type Questions</i>	5.29
6.	Amplifiers	6.1-6.85
6.1	Two-Port Devices and Network Parameters	6.1
6.2	The Hybrid Model for Two-port Network	6.3
6.3	Analysis of a Transistor Amplifier Circuit using <i>h</i> -parameters	6.7
6.4	Simplified CE Hybrid Model	6.15
6.5	Analysis of CC Amplifier using the Approximate Model	6.22
6.6	Analysis of CB Amplifier using the Approximate Model	6.25
6.7	Low Frequency Response of Transistor Amplifier	6.27
6.8	Effect of Coupling Capacitor C_C on Low Frequency Response	6.32
6.9	High Frequency π Model for a Transistor	6.33
6.10	The ' r_e ' Model of Transistor	6.40
6.11	Single Stage Amplifiers	6.44
6.12	Small Signal Analysis of Single Stage BJT Amplifiers	6.49
6.13	RC Coupled Amplifier	6.68

<i>Review Questions</i>	6.80
<i>Objective Type Questions</i>	6.83
7. Feedback Amplifiers	7.1-7.25
7.1 Introduction	7.1
7.2 Basic Concept of Feedback	7.1
7.3 Effects of Negative Feedback	7.3
7.4 Types of Negative Feedback Connections	7.7
7.5 Method of Identifying Feedback Topology and Feedback Factor	7.18
7.6 Stability of Feedback Amplifier	7.19
<i>Review Questions</i>	7.21
<i>Objective Type Questions</i>	7.23
8. Oscillators	8.1-8.42
8.1 Introduction	8.1
8.2 Classification of Oscillators	8.1
8.3 Conditions for Oscillation (Barkhausen Criterion)	8.2
8.4 General Form of an LC Oscillator	8.3
8.5 Hartley Oscillator	8.6
8.6 Colpitts Oscillator	8.9
8.7 Clapp Oscillator	8.12
8.8 Tuned Collector Oscillator	8.12
8.9 RC Oscillators	8.14
8.10 Wien-Bridge Oscillator	8.25
8.11 Twin-T-Oscillator	8.27
8.12 Crystal Oscillators	8.29
8.13 Miller Oscillator	8.32
8.14 Pierce Crystal Oscillator	8.33
8.15 Frequency Range of RC and LC Oscillators	8.33
8.16 Frequency Stability of Oscillator	8.34
8.17 Oscillators using FET	8.35
<i>Review Questions</i>	8.36
<i>Objective Type Questions</i>	8.38

Appendices

Appendix A: Specifications of Semiconductor Devices	A.1-A.11
Appendix B: Probable Value of General Physical Constants	B.1
Appendix C: Conversion Factors and Prefixes	C.1
Appendix D: Solutions to April/May 2008 Question Papers	D.1-D.7