

# Contents

<i>Preface to the Second Edition</i>	v
<i>Preface to the First Edition</i>	vii
<b>1. Elementary Concepts and Definitions</b>	<b>1</b>
1.1 Introduction	1
1.2 Work, Energy and Power	2
1.3 Basic Manifestations of Electricity	3
1.4 Electric Energy and Power	8
1.5 Superposition and Homogeneity	8
1.6 Ideal Circuit Elements	9
1.7 Fundamental Laws for Electric Circuits	19
1.8 Conclusion	26
<i>Additional Solved Problems</i>	27
<i>Problems</i>	29
<b>2. Fundamentals of Resistive Circuits</b>	<b>34</b>
2.1 Introduction	34
2.2 Series and Parallel Combinations of Resistances	34
2.3 Voltage and Current Division	36
2.4 Star (Y)–Delta ( $\Delta$ ) Conversion	39
2.5 Source Representation and Conversion	41
2.6 Nodal Analysis	43
2.7 Mesh Analysis	46
2.8 Dependent Sources	48
2.9 Network Theorems	50
2.10 Thevenin and Norton Theorems	51
<i>Additional Solved Problems</i>	58
<i>Problems</i>	61
<b>3. Fundamentals of Reactive Circuits</b>	<b>69</b>
3.1 Introduction	69
3.2 Inductance and Capacitance Combinations	69
3.3 Source-free RL and RC Circuits	72
3.4 Unit Step Forcing Function	77
3.5 Step Response of RL/RC Circuits	79
3.6 RLC Circuit	90
3.7 Circuit Response to Pulse and Impulse Excitations	102
<i>Additional Solved Problems</i>	105
<i>Problems</i>	110
<b>4. Steady State Analysis for Sinusoidal Excitation</b>	<b>116</b>
4.1 Introduction	116
4.2 Sinusoidal Function	116
4.3 Steady State Analysis-Phasor Method	123

4.4	Power in Sinusoidal Steady State	135
4.5	Nodal and Mesh Methods of Analysis	143
4.6	Network Theorems	146
4.7	Superposition of Average Power in AC Circuits	152
4.8	Sudden Application of Sinusoidal Excitation	154
	<i>Additional Solved Problems</i>	156
	<i>Problems</i>	162
<b>5.</b>	<b>More on Analysis of Circuits</b>	<b>169</b>
5.1	Introduction	169
5.2	Frequency Response of Simple Circuits	169
5.3	Bode Diagrams	172
5.4	Resonance	178
5.5	Fourier Series and Fourier Analysis	190
5.6	Two-Port Networks	194
	<i>Additional Solved Problems</i>	207
	<i>Problems</i>	211
<b>6.</b>	<b>Three-Phase Circuits</b>	<b>217</b>
6.1	Introduction	217
6.2	Three-Phase Voltages and Currents	217
6.3	Star Connection	219
6.4	Delta Connection	222
6.5	Equivalent Star of a Delta Connection	224
6.6	Three-phase Power	225
6.7	Three-phase Circuit Analysis	226
6.8	Star-Delta Conversion	227
	<i>Additional Solved Problems</i>	235
	<i>Problems</i>	238
<b>7.</b>	<b>Analysis of Circuits by Laplace Transformation</b>	<b>239</b>
7.1	Introduction	239
7.2	Laplace Transform	239
7.3	Properties of Laplace Transform	241
7.4	Laplace Transform Pairs and Table of Transforms	243
7.5	Laplace Transform Inversion	244
7.6	Partial Fraction Expansion	245
7.7	Initial and Final Value Theorems	248
7.8	Laplace Transform Circuit Analysis	249
7.9	Transformed Networks and Network Analysis	251
7.10	Impedance and Admittance	256
7.11	Network Function	258
7.12	Steady State Sinusoidal Response	262
	<i>Additional Solved Problems</i>	263
	<i>Problems</i>	267

<b>8. Magnetic Circuits</b>	<b>274</b>
8.1 Introduction	274
8.2 Magnetic Effects of Electric Current	275
8.3 Magnetic Circuits	276
8.4 Magnetic Materials and B–H Relationship (Magnetization Characteristic)	283
8.5 Electromagnetic Induction and Force	287
8.6 Inductance: Self and Mutual	289
8.7 Energy Stored in Magnetic Systems (Linear)	292
8.8 AC Operation of Magnetic Circuits	293
8.9 Hysteresis and Eddy-current Losses	296
<i>Additional Solved Problems</i>	298
<i>Problems</i>	300
<b>9. Transformers</b>	<b>303</b>
9.1 Introduction	303
9.2 Ideal Transformer (IT)	306
9.3 Accounting for Finite Permeability and Core Loss	311
9.4 Circuit Model of Transformer	314
9.5 Determination of Parameters of Circuit Model of Transformer	315
9.6 Per Unit System	318
9.7 Voltage Regulation	323
9.8 Efficiency	327
9.9 Autotransformer	329
9.10 Three-phase Transformers	332
9.11 Special Transformers	335
<i>Additional Solved Problems</i>	337
<i>Problems</i>	339
<b>10. EMF and Torque in Electric Machines</b>	<b>343</b>
10.1 Introduction	343
10.2 Rotating Machines	344
10.3 Elementary Synchronous Machine	347
10.4 Generated EMF of AC Windings	352
10.5 MMF of AC Winding	360
10.6 Rotating Magnetic Field	363
10.7 Torque in Round Rotor Machine	365
10.8 Basic Machine Types	367
10.9 Losses and Efficiency	373
10.10 Rating and Cooling	375
10.11 Matching Characteristics of Electric Machine and Load	377
<i>Additional Solved Problems</i>	379
<i>Problems</i>	381
<b>11. DC Machines</b>	<b>384</b>

11.1	Introduction	384	
11.2	Some Constructional Features	385	
11.3	EMF and Torque	388	
11.4	Circuit Model	391	
11.5	Armature Reaction	394	
11.6	Commutation	395	
11.7	Methods of Excitation and Magnetization Characteristics	396	
11.8	Characteristics of DC Motors and Speed Control	401	
11.9	DC Motor Starting	417	
11.10	Efficiency of DC Motors	418	
	<i>Additional Solved Problems</i>	420	
	<i>Problems</i>	422	
<b>12.</b>	<b>AC Machines</b>		<b>426</b>
12.1	Introduction	426	
12.2	Synchronous Machines	426	
12.3	Induction Machine	444	
12.4	Induction Generator	471	
	<i>Additional Solved Problems</i>	472	
	<i>Problems</i>	476	
<b>13.</b>	<b>Fractional-kW Motors</b>		<b>481</b>
13.1	Introduction	481	
13.2	Single-Phase Induction Motors	482	
13.3	Single-Phase Synchronous Motors	488	
13.4	AC Series Motor–Universal Motor	489	
<b>14.</b>	<b>Measurement Techniques and Electric and Electronic Instrumentation</b>		<b>492</b>
14.1	Introduction	492	
14.2	Electrical and Electronic Instruments	492	
14.3	Classification of Instruments	495	
14.4	Types of Indicating Instruments	497	
14.5	Instrument Transformer	513	
14.6	Bridge Measurements	514	
14.7	Electronic Voltmeter (EVMs)	520	
14.8	Electronic Multimeter (EMM)	524	
14.9	Measurement of Electronic Components	526	
14.10	Q-Meter	528	
14.11	Frequency Measurement	532	
14.12	Phase measurement	534	
14.13	Digital Instruments	534	
14.14	Transducers	544	
14.15	Oscilloscope	545	
14.16	Signal Generation, Signal Analysis and Fibre Optics Measurements	546	

14.17 Data Acquisition Systems	546
<i>Additional Solved Problems</i>	547
<i>Problems</i>	552
<b>15. Electric Energy</b>	<b>556</b>
15.1 Introduction	556
15.2 Energy Conversion	559
15.3 Thermal Power Generation— Steam/Gas-based	560
15.4 Nuclear Power Generation	566
15.5 Hydro Power	574
15.6 Magnetohydrodynamic (MHD) Generation	578
15.7 Geothermal Energy	579
15.8 Environmental Aspects of Electric Energy Generation	580
15.9 Renewable Energy Resources	585
15.10 Solar Energy and Its Utilization	586
15.11 Wind Power	602
15.12 Biofuels	609
15.13 Generating Reserve, Reliability and Certain Factors	610
15.14 Transmission and Distribution Systems	614
14.15 High Voltage DC (HVDC) Transmission	620
15.16 Energy Storage	624
15.17 Energy Conservation	627
15.18 Cost of Electricity Supply	629
<i>Solved Problems</i>	633
<b><i>Appendices</i></b>	<b>639</b>
Appendix A: Graph Theory	639
Appendix B: Answers to Problems	646
<b><i>Bibliography</i></b>	<b>656</b>
<b><i>Index</i></b>	<b>659</b>