

## **Contents**

*Visual Walkthrough*  
*Preface*

*vi*

*xv*

### **CHAPTER 1 AN INTRODUCTION TO ELECTRONICS 1**

- 1.1 Design Process 1
- 1.2 Signals 3
- 1.3 Voltage Amplifier and its Primary Parameters 8
- 1.4 Amplifier Parameters in Terms of Two-port Parameters 13
- 1.5 Need for Power Supplies in Electronic Circuits 16
- 1.6 Frequency Response of Amplifiers and Bandwidth 22
- 1.7 Bode Plots 27
- 1.8 Amplifier Transfer Functions 35
- 1.9 Mid Frequency Band 41
- 1.10 Difference and Operational Amplifiers 44
- 1.11 Sensitivity Analysis and Effects of Tolerance 56
- 1.12 Some Applications of Op-amps 64
- 1.13 Book Organization 67
  - Conclusions* 68
  - Reference* 69
  - Problems* 69

### **CHAPTER 2 SEMICONDUCTOR DIODES AND THEIR APPLICATIONS 77**

- 2.1 Ideal Diode 77
- 2.2 Semiconductor (Real) Diode 81
- 2.3 Analysis of Resistive Circuits with Diodes 89
- 2.4 Small-Signal Model of a Forward-biased Diode 96
- 2.5 Rectifiers 103
- 2.6 Limiting and Clamping Circuits 114
- 2.7 Zener Diodes and Shunt Voltage Regulator 117
  - Conclusions* 125
  - References* 126
  - Problems* 126

**CHAPTER 3 FIELD-EFFECT TRANSISTORS AND AMPLIFIERS 135**

- 3.1 MOSFETs: Structure and Operational Characteristics 136
- 3.2 Volt-ampere Relations and Large-signal Models 144
- 3.3 DC Analysis of FET Circuits 155
- 3.4 Constant Current Sources 167
- 3.5 A Conceptual Amplifier and Small-signal Models 174
- 3.6 IC Amplifiers with Passive Loads 182
- 3.7 IC Amplifiers with Active Loads 192
- 3.8 MOSFET Switches 203
- 3.9 FET Amplifiers—Discrete Circuits 212
  - Conclusions* 215
  - Problems* 215

**CHAPTER 4 BIPOLAR JUNCTION TRANSISTORS AND AMPLIFIERS 226**

- 4.1 Physical Operation of a BJT Under Active-mode 226
- 4.2 Ebers—Moll Equations and Large-signal Models 229
- 4.3 Analysis of Transistor Circuits with DC Sources 240
- 4.4 An Inverter Circuit 249
- 4.5 Small-signal Models of BJTs in the Active Mode 254
- 4.6 Basic IC Amplifier Configurations 259
- 4.7 Composite Transistor Amplifiers 274
- 4.8 Examples of Single-stage Discrete Amplifiers 281
- 4.9 Biasing Design in Discrete BJT Amplifiers 289
- 4.10 Complete Design Examples 296
  - Conclusions* 301
  - Problems* 301

**CHAPTER 5 DIFFERENCE AMPLIFIERS 315**

- 5.1 Improved Current Mirrors 315
- 5.2 Large-signal Analysis of Difference Amplifiers 327
- 5.3 Small-signal Analysis of BJT Difference Amplifiers with Passive Loads 337
- 5.4 MOSFET Difference Amplifier 348
- 5.5 Difference Amplifiers with Active Loads 351
- 5.6 Other Non-ideal Parameters of Difference Amplifiers 371
  - Conclusions* 377
  - Reference* 377
  - Problems* 377

**CHAPTER 6 POWER AMPLIFIERS AND OUTPUT STAGES 386**

- 6.1 Classification of Power Amplifiers 387
- 6.2 Class-A Power Amplifiers 388
- 6.3 Class-B Power Amplifiers 393
- 6.4 Class-AB Amplifiers 399
- 6.5 MOSFET Configurations 405
- 6.6 IC Power Operational Amplifiers 413
- 6.7 Power MOSFETs 415
  - Conclusions* 417
  - Problems* 417

**CHAPTER 7 MONOLITHIC IC AMPLIFIERS 421**

- 7.1 Level Shifting Amplifiers 421
- 7.2 CMOS Operational Amplifiers 424
- 7.3 BJT Operational Amplifiers 430
- 7.4 Analysis of 741-type Op-amp 432
- 7.5 Current-mode Amplifiers—Operational Transconductance Amplifier 442
- 7.6 Current Conveyors and Current-Feedback Amplifiers 448
  - Conclusions* 456
  - Problems* 456

**CHAPTER 8 FEEDBACK AMPLIFIERS 462**

- 8.1 Feedback Concept and Definitions 463
- 8.2 Four Basic Feedback Topologies 470
- 8.3 Analysis of the Series-shunt Configuration 474
- 8.4 Series-series Feedback Amplifier 481
- 8.5 Shunt-shunt Configuration 486
- 8.6 Shunt-series Configuration 487
  - Conclusions* 492
  - Problems* 493

**CHAPTER 9 FREQUENCY RESPONSES OF AMPLIFIERS 500**

- 9.1 Estimation of  $\omega_L$  and  $\omega_H$  using Short Circuit and Open Circuit Time Constants 501
- 9.2 Low Frequency Responses of Common-source (CS) and Common-emitter (CE)-amplifiers 504
- 9.3 High Frequency Models BJTs and MOSFETs 509
- 9.4 High-frequency Responses of CE- and CS-amplifiers 521
- 9.5 High Frequency Responses of Voltage Followers 532

---

9.6	High Frequency Responses of Current Followers	537
9.7	Frequency Response of Difference Amplifiers	542
9.8	Multistage Amplifier Examples	553
9.9	Frequency Responses of Monolithic IC Amplifiers	565
	<i>Conclusions</i>	574
	<i>Problems</i>	575

**CHAPTER 10 STABILITY ANALYSIS OF FEEDBACK AMPLIFIERS,  
FREQUENCY COMPENSATION, AND OSCILLATORS** **584**

10.1	Stability of Feedback Amplifiers	584
10.2	Frequency Compensation	593
10.3	Principle of Sinusoidal Oscillators and Barkhausen Criterion	606
10.4	Loop-gain Determination	608
10.5	Active-RC Sinusoidal Oscillators	609
10.6	Active-LC and Crystal Oscillators	621
	<i>Conclusion</i>	626
	<i>Problems</i>	626

**CHAPTER 11 ANALOG BUILDING BLOCKS** **632**

11.1	Instrumentation Amplifiers	633
11.2	Integrators	638
11.3	Differentiator	645
11.4	IC Multipliers—Gilbert Cell	648
11.5	Precision Rectifiers	654
11.6	Limiters	658
11.7	Comparators	665
11.8	Multivibrators and Waveform Generation	668
11.9	Digital-to-Analog Converters	675
11.10	Analog-to-Digital Converters	683
11.11	Voltage Regulators	688
11.12	Switched-mode DC/DC Converters	692
	<i>Conclusions</i>	702
	<i>Reference</i>	702
	<i>Problems</i>	702

**CHAPTER 12 FILTERS AND TUNED AMPLIFIERS** **711**

12.1	Filter Characteristics and Specifications	712
12.2	First and Second Order Filter Functions	716
12.3	Approximation Problem	722
12.4	First-order Filter Networks	735
12.5	Single-amplifier Second-order Filters	737

12.6	Double-integrator Loop Filters	744
12.7	GIC-based Multiple-amplifier Second-order Filters	749
12.8	Tuned Amplifiers	763
12.9	Active-SC Filters	772
	<i>Conclusions</i>	778
	<i>Reference</i>	778
	<i>Problems</i>	778
	<i>Answers to Selected Problems</i>	784
<b>Index</b>		<b>792</b>