

CONTENTS

Preface xv

CHAPTER 1

FIELD-EFFECT TRANSISTORS 1

- 1.1 Characteristics of the MOS Capacitor 3
 - 1.1.1 Accumulation Region 3
 - 1.1.2 Depletion Region 3
 - 1.1.3 Inversion Region 4
- 1.2 The NMOS Transistor 5
 - 1.2.1 Qualitative i - v Behavior of the NMOS Transistor 6
 - 1.2.2 Triode Region Characteristics of the NMOS Transistor 8
 - 1.2.3 On Resistance 11
 - 1.2.4 Use of the MOSFET as a Voltage-Controlled Resistor 12
 - 1.2.5 Saturation of the i - v Characteristics 13
 - 1.2.6 Mathematical Model in the Saturation (Pinch-Off) Region 14
 - 1.2.7 Transconductance 17
 - 1.2.8 Channel-Length Modulation 17
 - 1.2.9 Transfer Characteristics and Depletion-Mode MOSFETS 19
 - 1.2.10 Body Effect or Substrate Sensitivity 20
- 1.3 PMOS Transistors 22
- 1.4 MOSFET Circuit Symbols 24
- 1.5 MOS Transistor Fabrication and Layout Design Rules 27
 - 1.5.1 Minimum Feature Size and Alignment Tolerance 27
 - 1.5.2 MOS Transistor Layout 27
- 1.6 Capacitances in MOS Transistors 30
 - 1.6.1 NMOS Transistor Capacitances in the Triode Region 30
 - 1.6.2 Capacitances in the Saturation Region 31
 - 1.6.3 Capacitances in Cutoff 32
- 1.7 MOSFET Modeling in SPICE 32
- 1.8 Biasing the NMOS Field-Effect Transistor 34

- 1.9 Biasing the PMOS Field-Effect Transistor 53
- 1.10 Current Sources and the MOS Current Mirror 57
 - 1.10.1 dc Analysis of the NMOS Current Mirror 59
 - 1.10.2 Changing the MOS Mirror Ratio 61
 - 1.10.3 Output Resistance of the Current Mirror 62
 - 1.10.4 Current Mirror Layout 63
 - 1.10.5 Multiple Current Mirrors 64
- 1.11 MOS Transistor Scaling 68
 - 1.11.1 Drain Current 68
 - 1.11.2 Gate Capacitance 68
 - 1.11.3 Circuit and Power Densities 69
 - 1.11.4 Power-Delay Product 69
 - 1.11.5 Cutoff Frequency 70
 - 1.11.6 High Field Limitations 71
 - 1.11.7 Subthreshold Conduction 71
- 1.12 The Junction Field-Effect Transistor (JFET) (Advanced Topic) 72
 - 1.12.1 The JFET with Bias Applied 73
 - 1.12.2 JFET Channel with Drain-Source Bias 73
 - 1.12.3 n -Channel JFET i - v Characteristics 76
 - 1.12.4 The p -Channel JFET 77
 - 1.12.5 Circuit Symbols and JFET Model Summary 77
 - 1.12.6 JFET Capacitances 79
- 1.13 JFET MODELING IN SPICE 79
- 1.14 Biasing the JFET and Depletion-Mode MOSFET 80
 - Summary 83
 - Key Terms 85
 - References 86
 - Problems 86

CHAPTER 2

BIPOLAR JUNCTION TRANSISTORS 99

- 2.1 Physical Structure of the Bipolar Transistor 101

3.6.1	Voltage Amplifiers	210
3.6.2	Current Amplifiers	211
3.7	Amplifier Transfer Functions and Frequency Response	212
3.7.1	Bode Plots	213
3.7.2	The Low-Pass Amplifier	214
3.7.3	The High-Pass Amplifier	219
3.7.4	Band-Pass Amplifiers	222
3.7.5	Narrow-Band or High-Q Band-Pass Amplifiers	225
3.7.6	Band-Rejection Amplifiers	226
3.7.7	The All-Pass Function	227
3.7.8	More Complex Transfer Functions	228
	<i>Summary</i>	230
	<i>Key Terms</i>	231
	<i>References</i>	232
	<i>Problems</i>	232

CHAPTER 4

OPERATIONAL AMPLIFIERS 238

4.1	The Differential Amplifier	239
4.1.1	Differential Amplifier Model	240
4.1.2	The Ideal Differential Amplifier	242
4.2	The Ideal Operational Amplifier	243
4.2.1	Assumptions for Ideal Operational Amplifier Analysis	243
4.3	Analysis of Circuits Containing Ideal Operational Amplifiers	244
4.3.1	The Inverting Amplifier	244
4.3.2	The Noninverting Amplifier	248
4.3.3	The Unity-Gain Buffer, or Voltage Follower	251
4.3.4	The Summing Amplifier	253
4.3.5	The Difference Amplifier	254
4.3.6	The Instrumentation Amplifier	257
4.3.7	An Active Low-Pass Filter	259
4.3.8	The Integrator	262
4.3.9	Differentiation	263
4.3.10	Cascaded Amplifiers	264
4.3.11	Amplifier Terminology Review	266
4.4	Nonideal Operational Amplifiers	267
4.4.1	Finite Open-Loop Gain	267
4.4.2	Gain Error	269

4.4.3	Nonzero Output Resistance	270
4.4.4	Finite Input Resistance	275
4.4.5	Summary of Nonideal Inverting and Noninverting Amplifiers	279
4.4.6	Finite Common-Mode Rejection Ratio	279
4.4.7	Common-Mode Input Resistance	285
4.4.8	DC Error Sources	286
4.4.9	Output Voltage and Current Limits	292
4.5	Frequency Response and Bandwidth of Operational Amplifiers	297
4.5.1	Frequency Response of the Noninverting Amplifier	299
4.5.2	Inverting Amplifier Frequency Response	301
4.5.3	Frequency Response of Cascaded Amplifiers	304
4.5.4	Large-Signal Limitations—Slew Rate and Full-Power Bandwidth	312
4.5.5	Macro Model for Operational Amplifier Frequency Response	313
4.5.6	Complete Op Amp Macro Models in SPICE	314
4.5.7	Examples of Commercial General-Purpose Operational Amplifiers	314
	<i>Summary</i>	317
	<i>Key Terms</i>	318
	<i>References</i>	319
	<i>Additional Reading</i>	319
	<i>Problems</i>	319

CHAPTER 5

OPERATIONAL AMPLIFIER APPLICATIONS 334

5.1	Active Filters	335
5.1.1	Low-Pass Filter	335
5.1.2	Sensitivity	339
5.1.3	A High-Pass Filter with Gain	340
5.1.4	Band-Pass Filter	342
5.1.5	The Tow-Thomas Biquad	345
5.1.6	Magnitude and Frequency Scaling	349

5.2	Switched-Capacitor Circuits	351	6.4.1	Graphical Interpretation of the Small-Signal Behavior of the Diode	418
5.2.1	A Switched-Capacitor Integrator	351	6.4.2	Small-Signal Modeling of the Diode	420
5.2.2	Noninverting SC Integrator	353	6.4.3	A Current-Controlled Attenuator	422
5.2.3	Switched-Capacitor Filters	355	6.5	Small-Signal Models for Bipolar Junction Transistors	423
5.3	Digital-to-Analog Conversion	358	6.5.1	The Hybrid-Pi Model	426
5.3.1	D/A Converter Fundamentals	358	6.5.2	Small-Signal Current Gain	426
5.3.2	D/A Converter Errors	359	6.5.3	The Amplification Factor of the BJT	427
5.3.3	Digital-to-Analog Converter Circuits	362	6.5.4	Equivalent Forms of the Small-Signal Model	429
5.4	Analog-to-Digital Conversion	369	6.5.5	Definition of a Small Signal for the Bipolar Transistor	429
5.4.1	A/D Converter Fundamentals	370	6.5.6	Small-Signal Model for the pnp Transistor	431
5.4.2	Analog-to-Digital Converter Errors	371	6.5.7	ac Analysis Versus Transient Analysis in SPICE	432
5.4.3	Basic A/D Conversion Techniques	372	6.6	The BJT Common-Emitter (C-E) Amplifier	432
5.5	Nonlinear Circuit Applications	385	6.6.1	Voltage Gain of the Common-Emitter Amplifier	434
5.5.1	A Precision Half-Wave Rectifier	385	6.6.2	Model Simplifications	437
5.5.1	Nonsaturating Precision-Rectifier Circuit	386	6.6.3	A Design Guide for the Common-Emitter Amplifier with Resistive Load	438
5.5.3	An AC Voltmeter	387	6.6.4	Common-Emitter Voltage Gain Upper Bound	439
5.6	Circuits Using Positive Feedback	388	6.7	Small-Signal Models for Field-Effect Transistors	442
5.6.1	The Comparator and Schmitt Trigger	388	6.7.1	Small-Signal Model for the MOSFET	442
5.6.2	The Astable Multivibrator	391	6.7.2	Amplification Factor of the MOSFET	445
5.6.3	The Monostable Multivibrator or One Shot	393	6.7.3	Definition of Small-Signal Operation for the MOSFET	446
	Summary	395	6.7.4	Body Effect in the Four-Terminal MOSFET	447
	Key Terms	397	6.7.5	Small-Signal Model for the PMOS Transistor	448
	References	397	6.7.6	Small-Signal Model for the Junction Field-Effect Transistor	449
	Additional Reading	398	6.8	Summary and Comparison of the Small-Signal Models of the BJT and FET	451
	Problems	398	6.9	The Common-Source Amplifier	452
CHAPTER 6					
SMALL-SIGNAL MODELING AND LINEAR AMPLIFICATION 406					
6.1	The Transistor as an Amplifier	408			
6.1.1	The BJT Amplifier	408			
6.1.2	The MOSFET Amplifier	410			
6.2	Coupling and Bypass Capacitors	411			
6.3	Circuit Analysis Using dc and ac Equivalent Circuits	413			
6.3.1	Menu for dc and ac Analysis	414			
6.4	Introduction to Small-Signal Modeling	418			

6.9.1	Voltage Gain of the Common-Source Amplifier	452	7.1.4	Common-Collector (C-C) and Common-Drain (C-D) Topologies	508
6.9.2	A Design Guide for the Common-Source Amplifier with Resistive Load	458	7.1.5	Common-Base (C-B) and Common-Gate (C-G) Amplifiers	509
6.10	Input and Output Resistances of the Common-Emitter and Common-Source Amplifiers	460	7.2	Inverting Amplifiers—Common-Emitter and Common-Source Circuits	510
6.10.1	Common-Emitter Input Resistance	461	7.2.1	Terminal Voltage Gain	511
6.10.2	Common-Source Input Resistance	463	7.2.2	Input Resistance	512
6.10.3	Common-Emitter Output Resistance	464	7.2.3	Signal Source Voltage Gain	512
6.10.4	Common-Source Output Resistance	465	7.2.4	Important Limits	513
6.11	Examples of Common-Emitter and Common-Source Amplifiers	466	7.2.5	Output Resistance	517
6.11.1	A Common-Emitter Amplifier	466	7.2.6	Increased Signal Range	521
6.11.2	ac Versus Transient Analysis in SPICE—Another Visit	471	7.2.7	Satisfying the Condition $g_m R_E \gg 1$ or $g_m R_S \gg 1$	522
6.11.3	A MOSFET Common-Source Amplifier	472	7.2.8	Current Gain	523
6.11.4	A JFET Common-Source Amplifier	478	7.2.9	C-E/C-S Amplifier Summary	523
6.11.5	Comparison of the Three Amplifier Examples	482	7.2.10	Equivalent Transistor Representation of the Generalized C-E/C-S Transistor	524
6.11.6	Common-Emitter and Common-Source Amplifier Summary	483	7.3	Follower Circuits—Common-Collector and Common-Drain Amplifiers	525
6.11.7	Guidelines for Neglecting the Transistor Output Resistance	484	7.3.1	Terminal Voltage Gain	525
6.12	Amplifier Power and Signal Range	484	7.3.2	Input Resistance	527
6.12.1	Power Dissipation	484	7.3.3	Signal Source Voltage Gain	527
6.12.2	Signal Range	486	7.3.4	Follower Signal Range	529
	Summary	489	7.3.5	Output Resistance	530
	Key Terms	490	7.3.6	Current Gain	532
	Problems	491	7.3.7	C-C/C-D Amplifier Summary	533
CHAPTER 7			7.4	Noninverting Amplifiers—Common-Base and Common-Gate Circuits	534
SINGLE-TRANSISTOR AMPLIFIERS			503	7.4.1	Terminal Voltage Gain and Input Resistance
7.1	Amplifier Classification	504	7.4.2	Signal Source Voltage Gain	535
7.1.1	Signal Injection and Extraction—The BJT	505	7.4.3	Input Signal Range	539
7.1.2	Signal Injection and Extraction—The FET	506	7.4.4	Output Resistance	539
7.1.3	Generalized Common-Emitter (C-E) and Common-Source (C-S) Amplifiers	506	7.4.5	Current Gain	540
			7.4.6	C-B/C-G Amplifier Summary	541
			7.5	Amplifier Prototype Review and Comparison	542
			7.5.1	The BJT Amplifiers	542
			7.5.2	The FET Amplifiers	545
			7.6	Coupling and Bypass Capacitor Design	551
			7.6.1	Common-Emitter and Common-Source Amplifiers	551

7.6.2	Common-Collector and Common-Drain Amplifiers	556	8.3.4	ac Analysis of the Bipolar Differential Amplifier	627
7.6.3	Common-Base and Common-Gate Amplifiers	558	8.3.5	Differential-Mode Gain and Input Resistance	629
7.6.4	Setting Lower Cutoff Frequency f_L	562	8.3.6	Common-Mode Gain and Input Resistance	631
7.7	Amplifier Design Examples	563	8.3.7	Common-Mode Rejection Ratio (CMRR)	633
7.7.1	Monte Carlo Evaluation of the Common-Base Amplifier Design	573	8.3.8	Analysis Using Differential-and Common-Mode Half Circuits	634
7.8	The Influence of Body Effect on Amplifier Performance	579	8.3.9	Biasing with Electronic Current Sources	638
7.8.1	Common-Source Amplifier	579	8.3.10	Modeling the Electronic Current Source in SPICE	639
7.8.2	Common-Drain Amplifier	581	8.3.11	dc Analysis of the MOSFET Differential Amplifier	639
7.8.3	Common-Gate Amplifier	582	8.3.12	Differential-Mode Input Signals	641
	Summary	585	8.3.13	Small-Signal Transfer Characteristic for the MOS Differential Amplifier	642
	Key Terms	586	8.3.14	Common-Mode Input Signals	643
	Additional Reading	587	8.3.15	Two-Port Model for Differential Pairs	644
	Problems	587	8.4	Evolution to Basic Operational Amplifiers	646
CHAPTER 8					
MULTISTAGE AMPLIFIERS 601					
8.1	Multistage ac-Coupled Amplifiers	602	8.4.1	A Two-Stage Prototype for an Operational Amplifier	649
8.1.1	Voltage Gain	604	8.4.2	Improving the Op Amp Voltage Gain	655
8.1.2	Input Resistance	606	8.4.3	Output Resistance Reduction	656
8.1.3	Signal Source Voltage Gain	606	8.4.4	A CMOS Operational Amplifier Prototype	662
8.1.4	Output Resistance	607	8.4.5	BiCMOS Amplifiers	663
8.1.5	Current and Power Gain	608	8.5	Output Stages	664
8.1.6	Input Signal Range	609	8.5.1	The Source Follower—Class-A Output Stage	664
8.1.7	Improving Amplifier Voltage Gain	613	8.5.2	Source Follower with External Load Resistor	665
8.1.8	The Common-Emitter Cascade	613	8.5.3	Class-B Push-Pull Output Stage	667
8.2	Direct-Coupled Amplifiers	615	8.5.4	Class-AB Amplifiers	668
8.2.1	Analysis of a dc-Coupled Amplifier	615	8.5.5	Class-AB Output Stages for Operational Amplifiers	670
8.2.2	dc Analysis	616	8.5.6	Short-Circuit Protection	670
8.2.3	ac Analysis	619	8.5.7	Transformer Coupling	672
8.2.4	Compound Transistor Configurations—The Darlington and Cascode Circuits	620	8.6	Electronic Current Sources	676
8.3	Differential Amplifiers	623			
8.3.1	Bipolar and MOS Differential Amplifiers	624			
8.3.2	dc Analysis of the Bipolar Differential Amplifier	624			
8.3.3	Small-Signal Transfer Characteristic for the Bipolar Differential Amplifier	627			

- 8.6.1 Single-Transistor Current Sources 677
- 8.6.2 Figure of Merit for Current Sources 678
- 8.6.3 Higher Output Resistance Sources 679
- 8.6.4 Multiple Output Sources 680
- 8.6.5 Current Source Design Examples 682
- Summary 691
- Key Terms 693

CHAPTER 9

FREQUENCY RESPONSE 715

- 9.1 Amplifier Frequency Response 716
 - 9.1.1 Low-Frequency Response 717
 - 9.1.2 Estimating ω_L in the Absence of a Dominant Pole 718
 - 9.1.3 High-Frequency Response 721
 - 9.1.4 Estimating ω_H in the Absence of a Dominant Pole 721
- 9.2 Direct Determination of the Low-Frequency Poles and Zeros—The Common-Source Amplifier 723
- 9.3 Estimation of ω_L Using the Short-Circuit Time-Constant Method 728
 - 9.3.1 Estimate of ω_L for the Common-Emitter Amplifier 729
 - 9.3.2 Estimate of ω_L for the Common-Source Amplifier 734
 - 9.3.3 Estimate of ω_L for the Common-Base Amplifier 734
 - 9.3.4 Estimate of ω_L for the Common-Gate Amplifier 736
 - 9.3.5 Estimate of ω_L for the Common-Collector Amplifier 737
 - 9.3.6 Estimate of ω_L for the Common-Drain Amplifier 738
- 9.4 Transistor Models at High Frequencies 738
 - 9.4.1 Frequency-Dependent Hybrid-Pi Model for the Bipolar Transistor 738
 - 9.4.2 Modeling C_π and C_μ in SPICE 739
 - 9.4.3 Unity-Gain Frequency f_T 739
 - 9.4.4 High-Frequency Model for the FET 743
 - 9.4.5 Modeling C_{GS} and C_{GD} in SPICE 744
 - 9.4.6 Channel Length Dependence of f_T 744
 - 9.4.7 Limitations of the High-Frequency Models 746
- 9.5 Base Resistance in the Hybrid-Pi Model 747
 - 9.5.1 Effect of Base Resistance on Midband Amplifiers 747
- 9.6 High-Frequency Limitations of Common-Emitter and Common-Source Amplifiers 750
 - 9.6.1 Example of Direct High-Frequency Analysis—The Common-Emitter Amplifier 750
 - 9.6.2 Approximate Polynomial Factorization 752
 - 9.6.3 Poles of the Common-Emitter Amplifier—The CT Approximation 752
 - 9.6.4 Gain-Bandwidth Product Limitations of the Common-Emitter Amplifier 757
 - 9.6.5 Dominant Pole for the Common-Source Amplifier 758
- 9.7 Miller Multiplication 758
 - 9.7.1 Miller Integrator 760
- 9.8 Estimation of ω_H for Inverting Amplifiers, Noninverting Amplifiers, and Followers Using the Open-Circuit Time-Constant Method 762
 - 9.8.1 Gain-Bandwidth Trade-Off Using an Emitter Resistor 764
 - 9.8.2 Dominant Pole for the Common-Base Amplifier 768
 - 9.8.3 Dominant Pole of the Common-Gate Amplifier 770
 - 9.8.4 Dominant Pole for the Common-Collector Amplifier 771
 - 9.8.5 Dominant Pole for the Common-Drain Amplifier 774
 - 9.8.6 Single-Stage Amplifier High-Frequency Response Summary 774
- 9.9 Frequency Response of Multistage Amplifiers 775
 - 9.9.1 Differential Amplifier 775
 - 9.9.2 The Common-Collector Common-Base Cascade 778
 - 9.9.3 High-Frequency Response of the Cascode Amplifier 780

9.9.4	Cutoff Frequency for the Current Mirror	781	10.4.3	Output Resistance	840	
9.9.5	Three-Stage Amplifier Example	782	10.5	Current Amplifiers—Shunt-Series Feedback	845	
9.10	Single-Pole Operational Amplifier Compensation	789	10.5.1	Current Gain Calculation	845	
9.10.1	Three-Stage Op Amp Analysis	789	10.5.2	Input Resistance	846	
9.10.2	Transmission Zeros in FET Op Amps	792	10.5.3	Output Resistance	847	
9.10.3	Bipolar Amplifier Compensation	793	10.6	Transconductance Amplifiers—Series-Series Feedback	849	
9.10.4	Slew Rate of the Operational Amplifier	795	10.6.1	Transconductance Analysis	849	
9.10.5	Relationships Between Slew Rate and Gain-Bandwidth Product	796	10.6.2	Input and Output Resistances	851	
9.11	Tuned Amplifiers	797	10.7	Common Errors in Applying Two-Port Feedback Theory	851	
9.11.1	Single-Tuned Amplifier	797	10.8	Finding the Loop Gain	861	
9.11.2	Use of a Tapped Inductor—The Auto Transformer	800	10.8.1	Direct Calculation of the Loop Gain	861	
9.11.3	Multiple Tuned Circuits—Synchronous and Stagger Tuning	802	10.8.2	Finding the Loop Gain Using Successive Voltage and Current Injection	862	
9.12	Mixers and Balanced Modulators	804	10.8.3	Simplifications	866	
9.12.1	A Single-Balanced Mixer	804	10.9	Blackman's Theorem to the Rescue	869	
9.12.2	The Gilbert Multiplier as a Double-Balanced Mixer/Modulator	806	10.10	Using Feedback to Control Frequency Response	876	
9.12.3	Conversion Gain	808	10.11	Stability of Feedback Amplifiers	878	
	<i>Summary</i>	809	10.11.1	The Nyquist Plot	878	
	<i>Key Terms</i>	810	10.11.2	First-Order Systems	878	
	<i>References</i>	811	10.11.3	Second-Order Systems and Phase Margin	880	
	<i>Problems</i>	811	10.11.4	Third-Order Systems and Gain Margin	881	
			10.11.5	Determining Stability from the Bode Plot	882	
CHAPTER 10			10.12	Oscillators	891	
FEEDBACK, STABILITY, AND OSCILLATORS			824	10.12.1	The Barkhausen Criteria for Oscillation	891
10.1	Classic Feedback Systems	825	10.12.2	Oscillators Employing Frequency-Selective RC Networks	892	
10.2	Feedback Amplifier Design Using Two-Port Network Theory	826	10.12.3	LC Oscillators	896	
10.3	Voltage Amplifiers—Series-Shunt Feedback	827	10.12.4	Crystal Oscillators	900	
10.3.1	Voltage Gain Calculation	828		<i>Summary</i>	905	
10.3.2	Input Resistance	831		<i>Key Terms</i>	906	
10.3.3	Output Resistance	831		<i>References</i>	906	
10.4	Transresistance Amplifiers—Shunt-Shunt Feedback	836		<i>Problems</i>	907	
10.4.1	Transresistance Analysis	836	APPENDIXES			
10.4.2	Input Resistance	839	A	Standard Discrete Component Values	915	
			B	Solid-State Device Models and SPICE Simulation Parameters	922	
				Index	929	