

Contents

Preface

xv

1. ESSENTIAL BASICS 1

Part I Basic Electrical Terms and Components

- 1.1 Basic Electrical Terms 1
- 1.2 Series and Parallel Circuits 2
- 1.3 Electrical Components 4

Part II Basic Magnetic Terms and Components

- 1.4 Basic Magnetic Terms 7
- 1.5 Magnetic Materials 10
- 1.6 Transformer Types and Frequency Ranges 10
- 1.7 Inductors 11
- 1.8 Stray Capacitances and Inductances 15
- 1.9 High Frequency Small-signal Models of Linear Passive Elements 16
- 1.10 Transformers 18
- 1.11 Voltage and Current Sources 21
- 1.12 Dependent and Independent Sources 23
- 1.13 Miscellaneous Terms in Circuit Analysis 24
- 1.14 Active and Passive Circuits 25
- 1.15 AC Circuits 25
- 1.16 Circuit Analysis Laws 27
- 1.17 Circuit Analysis Theorems 27
- 1.18 Classification of Signals 29
- 1.19 Fundamentals of Analog Amplification 302

Part III Measurements and Basic Laboratory Equipments

- 1.20 Basic Measurement Terms 31
- 1.21 Voltage and Current Measurements 31
- 1.22 AC Measurements 32
- 1.23 Resistance Measurement 32
- 1.24 Analog Multimeters 32
- 1.25 Digital Multimeters (DMMs) 33
- 1.26 Cathode Ray Oscilloscopes (CRO) 33

viii Contents

- 1.27 Oscilloscope Controls 36
- 1.28 Coupling Options 38
- 1.29 Measurements Using Oscilloscopes 40
- 1.30 Signal Generators 42
- 1.31 Function Generators 43
- 1.32 Power Supplies 43
- 1.33 Printed Circuit Boards 44
- Review Questions 47

2. SEMICONDUCTOR PHYSICS 51

- 2.1 Introduction 51
- 2.2 An Ideal Atom 51
- 2.3 Ionization 53
- 2.4 Crystals and Atomic Bonding 53
- 2.5 Energy Band Theory of Crystals 54
- 2.6 Classification of Materials Based on Energy Bands—Conductors
Semiconductors and Insulators 54
- 2.7 Intrinsic Semiconductors 56
- 2.8 Extrinsic Semiconductors 59
- 2.9 Thermal Equilibrium 61
- 2.10 Fermi Level 62
- 2.11 The Mass Action Law 65
- 2.12 Charge Densities in a Semiconductor 66
- 2.13 Conduction Mechanisms in a Semiconductor 68
- 2.14 Total Current Density 70
- 2.15 Einstein Relationship 71
- 2.16 Conductivity of a Semiconductor 71
- 2.17 The Hall Effect 80
- 2.18 Excess Carriers 82
- 2.19 Metal–Semiconductor Junction—An Ohmic Contact 83
- 2.20 Compound Semiconductor Materials 83
- 2.21 Direct and Indirect Bandgap Semiconductors 84
- Review Questions 91

3. DIODES AND THEIR APPLICATIONS 93

Part I Diodes

- 3.1 Introduction and Overview 93
- 3.2 p-n junction Diode 94
- 3.3 Diode Capacitances 98
- 3.4 A Linearly Graded Junction 103
- 3.5 Ohmic Contacts 103
- 3.6 Ideal V - I Characteristics of p-n Junction Diodes 104
- 3.7 DC or Static Resistance of Diode 107
- 3.8 AC or Dynamic Resistance 107
- 3.9 Temperature Dependence of V - I Characteristics 109

- 3.10 Small-signal and Large-signal (Piecewise Linear Approximation) Diode Models 111
- 3.11 DC Load Line 113
- 3.12 Voltage Breakdowns in Diodes 114
- 3.13 Important Diode Data Sheet Specifications 115

Part II Diode Applications

- 3.14 Diodes in DC Circuits 117
- 3.15 Problem Solving Technique for Circuit Containing Diodes Resistances and DC Sources 118
- 3.16 Problem Solving Techniques 132
- 3.17 Voltage Multiplier Circuits 141
- 3.18 Voltage Doubler 141
- 3.19 Rectifier Circuits 144
- 3.20 Conventions and Symbols Used in Analysis of Rectifier Circuits 148

Part III Special Purpose Diodes

- 3.21 Zener Diodes 166
- 3.22 Light Emitting Diodes (LED) 172
- 3.23 Photodiodes 174
- 3.24 Tunnel Diode 174
- 3.25 IMPATT Diodes 175
- 3.26 Gunn Diode 177
- 3.27 Varactor Diodes 178
- 3.26 Schottky Diodes 178
- 3.29 RF DIODES 180
- Review Questions 199

4. FIELD EFFECT TRANSISTORS AND THEIR APPLICATIONS 203

Part I Junction Field Effect Transistors

- 4.1 Introduction 203
- 4.2 Junction Field Effect Transistors 204

Part II Junction Field Effect Transistor Applications

- 4.3 JFET Amplifiers 220
- 4.4 FET Small-signal Model 220
- 4.5 JFET as an Amplifier 223

Part III Metal Oxide Semiconductor Field Effect Transistors (MOSFETs)

- 4.6 An Overview 236
- 4.7 Basics of MOS Transistor Operation 237
- 4.8 Construction of n-Channel EMOSFET 238
- 4.9 EMOSFET Symbols 239
- 4.10 EMOSFET Working 240
- 4.11 EMOSFET Transfer Characteristics 244
- 4.12 Non-Ideal $V-I$ Characteristics 245

- 4.13 Important Data Sheet Specifications of EMOSFET 250
- 4.14 MOSFET Handling Precautions 250
- 4.15 Depletion MOSFET (DMOSFET) 251
- 4.16 MOSFET Biasing 253
- 4.17 Power MOSFET 255
- 4.18 Metal-Semiconductor Field Effect Transistor (MESFET) 256

Part IV MOSFET Applications

- 4.19 MOSFET Small-signal Amplifiers 257
- 4.20 MOSFET Application in Digital Logic 260
- 4.21 Introduction to EMOSFET as Basic Element in VLSI 262
- 4.22 MOSFET Scaling and Small Geometry Effects 263
- 4.23 Small Geometry Effects 266
- 4.24 CMOS Inverter 268
- Review Questions* 288

5. BIPOLAR JUNCTION TRANSISTOR AND THEIR APPLICATIONS

290

Part I Bipolar Junction Transistor

- 5.1 Introduction and Overview 290
- 5.2 BJT Construction 291
- 5.3 Symbols and Conventions 292
- 5.4 BJT Working 292
- 5.5 Transistor Currents 294
- 5.6 Transistor Configurations and Input/Output Characteristics 297
- 5.7 CB Configuration—Three Regions of Operations—Active, Saturation and Cut-off 301
- 5.8 CE Configuration 302
- 5.9 CE Configuration—Three Regions of Operations—Active, Saturation and Cut-off 304
- 5.10 CC Configuration 307
- 5.11 Ebers Moll Model 309
- 5.12 Modes of Operation of Transistor and Application of EM Model 310
- 5.13 Transistor as an Amplifier 313
- 5.14 Transistor as a Switch 316
- 5.15 Transistor Parameters and Data Sheets Specifications 318
- 5.16 BJT Packaging and Terminal Identification 322

Part II BJT Applications

- 5.17 BJT Small-signal Low Frequency Amplifiers 323
- 5.18 BJT Biasing and Small-signal Amplifiers 324
- 5.19 BJT Biasing 340
- 5.20 Biasing Arrangements 342
- 5.21 Thermal Stabilization 345
- 5.22 Bias Compensation 346
- 5.23 Thermal Runaway 348

5.24	Biasing Techniques for Integrated Circuits	348
5.25	Current Sources and Current Mirrors	350
5.26	BJT Small-signal Low Frequency Amplifiers	353
5.27	Small-signal Amplifier Performance in Terms of h-parameters	361
5.28	Practical Transistor Amplifiers	365
5.29	Method of Deriving DC and AC Small-signal Equivalent Circuit for a given Amplifier	367
5.30	Approximate Analysis of BJT Amplifiers using h-parameters	383
5.31	Comparison of CE, CC and CB Configurations	384
5.32	High Input Impedance BJT Amplifier Configurations	388
5.33	Biasing Problem	390
5.34	Small-signal Hybrid- π model	398
5.35	Multi Stage Amplifiers	399
5.36	Analysis of Multistage Amplifiers	402
5.37	BJT Low Frequency Large-signal Amplifiers	409
5.38	Class A Amplifier	412
5.39	Class B Amplifier	416
5.40	Class AB Amplifier	423
5.41	Distortion in Amplifiers	430
5.42	Graphical Analysis of Distortion	431
5.43	Power Output and Distortion for Transformer Coupled Class A Amplifier	435
5.44	Power BJTs	436
5.45	Introduction to High Efficiency Power Amplifiers (Class C, Class D and Class S Amplifiers)	437
5.46	High Frequency BJT	438
5.47	Comparison of BJT and FET	449
5.48	Heterojunction Bipolar Transistors	450
	Review Questions	476

6. OPERATIONAL AMPLIFIERS AND THEIR APPLICATIONS 478

Part I Operational Amplifiers

6.1	Introduction	478
6.2	An Ideal OPAMP	479
6.3	Linear OPAMP Circuits	481
6.4	Practical OPAMPS, Parameters and their Measurements	486
6.5	Differential Amplifier	506
6.6	Current Mirror	508
6.7	Open Loop Operation of OPAMPS	510
6.8	Introduction to BiCMOS Technology	510
6.9	BiCMOS Analog Circuits	511

Part II OPAMP Applications

6.10	Linear Applications of OPAMPS	513
6.11	Integrator	521

- 6.12 Differentiator 524
- 6.13 Non-linear OPAMP Circuits 526
- 6.14 Introduction to Instrumentation and Isolation Amplifiers 530
- 6.15 Choice of OPAMP for given Application 533
- Review Questions* 543

7. FREQUENCY RESPONSE 545

- 7.1 Introduction 545
- 7.2 Basic Concepts 546
- 7.3 Human Ear Response 549
- 7.4 Square Wave Testing of Amplifiers 551
- 7.5 Analysis of Output Waveform 552
- 7.6 Bode Plots 555
- 7.7 Frequency Response of RC-Coupled Amplifier 558
- 7.8 RC-Coupled Amplifiers 560
- 7.9 Effect of Coupling and Emitter Bypass Capacitors on Frequency Response 564
- 7.10 Gain Bandwidth Product (GBW) 568
- 7.11 Effect of Cascading on Frequency Response 568
- 7.12 Total Frequency Response of an Amplifier and Concept of Dominant Pole 574
- Review Questions* 583

8. FEEDBACK AND OSCILLATORS 584

Part I Feedback

- 8.1 Introduction 584
- 8.2 A Generalized Feedback Amplifier 585
- 8.3 Four Basic Amplifier Types and Feedback Topologies 587
- 8.4 Desirable Characteristics of Four Basic Amplifiers 588
- 8.5 Effect of Feedback on Amplifier Performance 591
- 8.6 Improved Input and Output Resistances 596
- 8.7 Feedback Amplifier Circuits and their Analysis 604
- 8.8 Generic Method for Analysis of Feedback Amplifiers 604
- 8.9 Voltage-series Feedback Topology 605
- 8.10 Current-series Feedback Topology 615
- 8.11 Current-shunt Feedback Topology 621
- 8.12 Voltage-shunt Feedback Topology 625

Part II Oscillators

- 8.13 Introduction 629
- 8.14 Stability of Systems with Feedback 630
- 8.15 Gain and Phase Margins 631
- 8.16 Positive Feedback and Oscillators 632
- 8.17 RC Oscillators 635
- 8.18 LC Oscillators 642

8.19	Crystal Oscillators	649
8.20	Frequency Stability of Oscillators	653
8.21	Crystal Clock	654
	<i>Review Questions</i>	674

9. LINEAR VOLTAGE AND VOLTAGE REFERENCES 676

9.1	Introduction and Overview	676
9.2	The Unregulated Power Supply	677
9.3	Filters in Power Supplies	677
9.4	Linear Regulators and their Performance Parameters	685
9.5	Series Regulators	688
9.6	Power Supply Protection	700
9.7	Shunt Regulators	706
9.8	IC Regulators	707
9.9	Regulator Circuits	714
9.10	Voltage References	717
	<i>Review Questions</i>	728

APPENDICES

<i>Appendix 1.</i>	Physical Constants	730
<i>Appendix 2.</i>	Resistors: Standard Values, Tolerance and Resistor Series	731
<i>Appendix 3.</i>	Selection Guidelines for Resistors	739
<i>Appendix 4.</i>	Capacitors: Selection Guidelines and Applications	742
<i>Appendix 5.</i>	Properties of Commonly used Semiconductor Materials	747
<i>Appendix 6.</i>	Transistor Data Sheets and their Interpretation	748
<i>Appendix 7.</i>	Common Mode Signals, Grounding, Shielding	749
<i>Appendix 8.</i>	Introduction to Circuit Simulation	753
<i>Appendix 9.</i>	IEEE Frequency Spectrum	762
	<i>References and Further Reading</i>	763
	<i>Index</i>	764