

# Contents

---

<i>Preface to the Second Edition</i>	<i>xv</i>
<i>Preface to the First Edition</i>	<i>xxi</i>
<b>1. Review of Selected Topics in Electronic Circuit Theory</b>	<b>1</b>
1.1 Network Theorems	1
1.2 IEEE Notation	4
1.3 Low-frequency Small-signal Transistor Model	6
1.4 The Hybrid- $\pi$ , High-frequency, Small-signal, Common-emitter Model	9
1.5 Voltage and Current Amplifications	10
1.6 Miller's Theorem	14
1.7 The Operational Amplifier	15
1.8 A Current Feedback Amplifier	19
1.9 Input and Output Impedance of a Transistor Stage	21
<i>Review Questions</i>	23
<i>Problems</i>	24
<b>2. Linear Waveshaping RC, RL, and RLC Circuits</b>	<b>27</b>
2.1 High-Pass RC Circuit	27
2.2 High-Pass RC Circuit: Exponential and Ramp Inputs	37
2.3 High-Pass RC Circuit as a Differentiator	42
2.4 Double Differentiation	45
2.5 Low-Pass RC Circuit	46
2.6 Low-Pass RC Circuit (Exponential and Ramp Inputs)	53
2.7 Low-Pass RC Circuit as an Integrator	56
2.8 Attenuators	57
2.9 RL Circuits	62
2.10 RLC Circuits	64
2.11 Ringing Circuit	68
<i>Review Questions</i>	69
<i>Problems</i>	71
<b>3. Wide Band Amplifiers</b>	<b>76</b>
3.1 Frequency Response of an Amplifier	77
3.2 Step Response of an Amplifier	78
3.3 RC-Coupled Amplifier	80
3.4 Low-Frequency Response of an RC-Coupled Stage	80
3.5 Frequency Response of a Transistor Stage—The Short-Circuit Current Gain	83
3.6 Current Gain with Resistive Load	87
3.7 Transistor Amplifier Response taking Source Impedance into Account	88
3.8 Transient Response of a Transistor Stage	94
3.9 Cascaded CE Transistor Stages	95

3.10	Rise-time Response of Cascaded Stages	99
3.11	Shunt Compensation of a Transistor Stage in a Cascade	101
3.12	Rise Time of Cascaded Compensated Stages	107
3.13	Low-Frequency Compensation	108
3.14	High-Frequency Response of a Stage with an Emitter Impedance	112
	<i>Review Questions</i>	116
	<i>Problems</i>	120
<b>4.</b>	<b>Steady-state Switching Characteristics of Devices</b>	<b>123</b>
4.1	The Semiconductor Diode	123
4.2	The Temperature Dependence of $p$ - $n$ Characteristics	128
4.3	Diode Transition Capacitance	131
4.4	Avalanche Diode	132
4.5	Diode Resistance	135
4.6	The Transistor as a Switch	136
4.7	The Transistor at Cut-off	138
4.8	The Transistor Switch in Saturation	142
4.9	Input Characteristics	144
4.10	Analysis of Cut-off and Saturation Regions	147
4.11	Typical Transistor-Junction Voltage Values	149
	<i>Review Questions</i>	150
	<i>Problems</i>	151
<b>5.</b>	<b>Clipping and Comparator Circuits</b>	<b>154</b>
5.1	Clipping (Limiting) Circuits	154
5.2	Diode Clippers	155
5.3	The Transistor Clipper	160
5.4	Clipping at Two Independent Levels	162
5.5	Comparators	165
5.6	Breakaway Diode and Amplifier	167
5.7	Diode-Differentiator Comparator	168
5.8	Applications of Voltage Comparators	171
	<i>Review Questions</i>	172
	<i>Problems</i>	173
<b>6.</b>	<b>Clamping and Switching Circuits</b>	<b>178</b>
6.1	The Clamping Operation	178
6.2	Clamping Circuit Taking Source and Diode Resistances into Account	181
6.3	A Clamping-Circuit Theorem	185
6.4	Practical Clamping Circuits	188
6.5	Effect of Diode Characteristics on Clamping Voltage	191
6.6	Synchronized Clamping	194
6.7	Transistor Switch with Inductive Load	196
6.8	Damper Diodes	198
6.9	Transistor Switch with Capacitive Load	198

---

6.10	Collector Catching Diodes	200	
6.11	Nonsaturating Switches	202	
6.12	The Emitter Follower with a Capacitive Load	204	
	<i>Review Questions</i>	206	
	<i>Problems</i>	206	
<b>7.</b>	<b>Logic Circuits</b>		<b>211</b>
7.1	Some Features of a Digital Computer	211	
7.2	Binary Operation of a System	213	
7.3	The OR Gate	217	
7.4	The AND Gate	222	
7.5	The NOT or Inverter Circuit	226	
7.6	The Inhibit Operations	229	
7.7	The Exclusive OR Circuit	231	
7.8	De Morgan's Laws	233	
7.9	The NAND and NOR Gates (DTL Logic)	236	
7.10	Two Logic-Circuit Conversion Theorems	240	
7.11	Packaging of Logic Circuits	241	
7.12	Binary Addition	243	
7.13	Registers	247	
7.14	Dynamic Registers	251	
7.15	Diode Matrices or Code-Operated Switches	253	
7.16	Resistor-Transistor Logic <sup>2</sup> (RTL and RCTL)	257	
7.17	Direct-Coupled Transistor Logic (DCTL)	259	
7.18	Low-Level Logic (DTL and TTL)	260	
7.19	Current-Mode Logic (CML or ECTL)	261	
7.20	Comparison of Logic Circuits	262	
	<i>Review Questions</i>	262	
	<i>Problems</i>	264	
<b>8.</b>	<b>Bistable Multivibrators</b>		<b>270</b>
8.1	The Stable States of a Bistable Multivibrator	270	
8.2	A Fixed-Bias Transistor Bistable Multivibrator	271	
8.3	A Self-biased Transistor Bistable Multivibrator	276	
8.4	Commutating Capacitors	279	
8.5	Methods of Improving Resolution	282	
8.6	Unsymmetrical Triggering of the Bistable Multivibrator	283	
8.7	Triggering Unsymmetrically Through a Unilateral Device	285	
8.8	Symmetrical Triggering	287	
8.9	A Direct-Connected Bistable Multivibrator Circuit	289	
8.10	Schmitt Trigger Circuit	291	
8.11	An Emitter-Coupled Bistable Multivibrator	295	
	<i>Review Questions</i>	300	
	<i>Problems</i>	301	
<b>9.</b>	<b>Monostable and Astable Multivibrators</b>		<b>305</b>
9.1	The Monostable Multivibrator	305	

---

9.2	Gate Width of a Collector-Coupled Monostable Multivibrator	309
9.3	Waveforms of the Collector-Coupled Monostable Multivibrator	311
9.4	The Emitter-Coupled Monostable Multivibrator	315
9.5	Gate Width of an Emitter-Coupled Monostable Multivibrator	322
9.6	The Influence of $V$ on Waveforms	323
9.7	Triggering of the Monostable Multivibrator	324
9.8	The Monostable Circuit Adjusted for Free-Running Operation	325
9.9	The Astable Collector-Coupled Multivibrator	326
9.10	The Astable Emitter-coupled Multivibrator	330
	<i>Review Questions</i>	335
	<i>Problems</i>	336
<b>10.</b>	<b>Negative-Resistance Devices</b>	<b>340</b>
10.1	The Tunnel Diode	340
10.2	The Backward Diode	343
10.3	The Unijunction Transistor	344
10.4	The Four-Layer Diode	347
10.5	$p$ - $n$ - $p$ - $n$ Characteristics	350
10.6	The Silicon Controlled Switch	352
10.7	SCS Characteristics	354
10.8	Additional Four-Layer Devices	357
10.9	The Thyristor	357
10.10	Avalanche-Mode Operation of Transistors	358
	<i>Review Questions</i>	359
	<i>Problems</i>	359
<b>11.</b>	<b>Negative-Resistance Switching Circuits</b>	<b>363</b>
11.1	The Negative-Resistance Characteristic	363
11.2	Basic Circuit Principles	364
11.3	Monostable Operation	366
11.4	Bistable Operation	367
11.5	Astable Operation	368
11.6	Voltage-Controlled Negative-Resistance Switching Circuits	369
11.7	Tunnel-Diode Monostable Circuit	371
11.8	Tunnel-Diode Astable Circuit	374
11.9	Tunnel-Diode Comparator	376
11.10	Tunnel-Diode Bistable Circuit	377
11.11	Tunnel-Diode—Transistor Hybrid Circuits	378
11.12	Circuit Applications of $p$ - $n$ - $p$ - $n$ Diodes	380
11.13	Applications of the Unijunction Transistor	383
11.14	Silicon-Controlled-Switch Circuits	388
	<i>Review Questions</i>	389
	<i>Problems</i>	390
<b>12.</b>	<b>Voltage Time-Base Generators</b>	<b>398</b>
12.1	General Features of a Time-Base Signal	398

12.2	Methods of Generating a Time-Base Waveform	399
12.3	Exponential Sweep Circuit	400
12.4	Negative-Resistance Switches	401
12.5	Sweep Circuit Using a Transistor Switch	405
12.6	A Fixed-Amplitude Sweep	408
12.7	A Transistor Constant-Current Sweep	409
12.8	Miller and Bootstrap Time-Base Generators—General Considerations	412
12.9	The Transistor Miller Time-Base Generator	416
12.10	Bootstrap Time-Base Generators—Basic Principles	419
12.11	The Transistor Bootstrap Time-Base Generator	422
	<i>Review Questions</i>	430
	<i>Problems</i>	431
<b>13.</b>	<b>Current Time-Base Generators</b>	<b>438</b>
13.1	A Simple Current Sweep	438
13.2	Linearity Correction through Adjustment of Driving Waveform	440
13.3	A Transistor Current Time-Base Generator	442
13.4	Coil Capacitance	447
13.5	Effect of the Omission of the Impulse Component of Current	449
13.6	Methods of Linearity Improvement	451
13.7	Illustrative Current Sweep Circuits	453
	<i>Review Questions</i>	455
	<i>Problems</i>	455
<b>14.</b>	<b>Pulse Transformers and Blocking Oscillators</b>	<b>459</b>
14.1	Pulse-Transformer Applications	459
14.2	Transformer Models	460
14.3	Complete Equivalent Circuit	463
14.4	Transformer Inductances	464
14.5	Transformer Capacitances	466
14.6	Rise-Time Response of a Transformer	467
14.7	The Flat Top of the Pulse	469
14.8	Complete Pulse Response of a Transformer	470
14.9	A Triggered Transistor Blocking Oscillator (Base Timing)	473
14.10	A Triggered Transistor Blocking Oscillator (Emitter Timing)	476
14.11	Additional Methods for Controlling the Pulse Duration of a Blocking Oscillator	481
14.12	The Blocking-Oscillator Rise Time	483
14.13	An Astable Transistor Blocking Oscillator (Diode-Controlled)	484
14.14	An Astable Transistor Blocking Oscillator (RC-Controlled)	488
14.15	Applications of Blocking Oscillators	491
	<i>Review Questions</i>	491
	<i>Problems</i>	492
<b>15.</b>	<b>Sampling Gates</b>	<b>500</b>
15.1	Basic Operating Principle of Gates	500

15.2	Unidirectional Diode Gate	501	
15.3	Other Forms of the Unidirectional Diode Gate	503	
15.4	Bidirectional Gates Using Transistors	505	
15.5	Reduction of Pedestal in a Gate Circuit	505	
15.6	A Bidirectional Diode Gate	507	
15.7	Balance Conditions in a Bidirectional Diode Gate	510	
15.8	Signal-Input Resistance and Connections	512	
15.9	Four-Diode Gate	512	
15.10	An Alternative Form of Four-Diode Gate	514	
15.11	Six-Diode Gate	515	
15.12	Chopper Amplifiers	516	
15.13	The Transistor as a Chopper Switch—ON State	518	
15.14	Transistor Chopper—OFF State	521	
15.15	Balanced Choppers	523	
15.16	Sampling Scope	525	
	<i>Review Questions</i>	527	
	<i>Problems</i>	527	
<b>16.</b>	<b>Counting and Timing</b>		<b>532</b>
16.1	A Cascade of Bistable Multivibrators as a Counter	532	
16.2	A Reversible Binary Counter	535	
16.3	Application of Counters	535	
16.4	Counting to a Base not a Power of 2	538	
16.5	Decade Counter without Feedback	541	
16.6	Carry Time in a Bistable Multivibrator Chain	542	
16.7	Improvement of Resolutions	544	
16.8	Vernier Counting	545	
16.9	Counters Using Current-Controlled Negative-Resistance Devices	548	
16.10	Ring Counters	549	
16.11	Storage Counters	552	
16.12	Applications of Storage Counters	557	
	<i>Review Questions</i>	557	
	<i>Problems</i>	558	
<b>17.</b>	<b>Synchronization and Frequency Division</b>		<b>561</b>
17.1	Pulse Synchronization of Relaxation Devices	561	
17.2	Frequency Division in the Sweep Circuit	563	
17.3	Other Astable Relaxation Circuits	565	
17.4	Monostable Relaxation Circuits as Dividers	568	
17.5	Stability of Relaxation Dividers	569	
17.6	Synchronization of a Sweep Circuit with Symmetrical Signals	571	
17.7	Sine-wave Frequency Division with a Sweep Circuit	575	
17.8	A Sinusoidal Divider using Regeneration and Modulation	576	
	<i>Review Questions</i>	578	
	<i>Problems</i>	578	

---

<b>18. Transient Switching Characteristics of Diodes and Transistors</b>	<b>581</b>
18.1 Diode Forward Recovery Time	581
18.2 Diode Reverse Recovery Time	584
18.3 Diode Storage and Transition Times	587
18.4 Charge–Storage–Diode Pulse Generator	588
18.5 Semiconductor–Metal Junction Diodes	590
18.6 Charge Compensation for Minimizing Storage Time	590
18.7 Transistor Switching Times	593
18.8 The Delay Time	595
18.9 The Rise Time	597
18.10 Storage Time	600
18.11 The Fall Time	605
18.12 Charge–Control Description of Transistor Behaviour	606
18.13 Stored Base Charge as a Parameter	609
18.14 The <i>RCTL</i> Switch	611
<i>Review Questions</i>	612
<i>Problems</i>	612
<b>Appendix 1: Ringing Circuit with Non-zero Initial Conditions</b>	<b>617</b>
<i>Bibliography</i>	620
<i>Index</i>	627