

Contents

Preface xii

Acknowledgments xvi

Guided Tour xx

A Note to the Student xxiii

About the Authors xxv

PART 1 DC Circuits 2

Chapter 1 Basic Concepts 3

- 1.1 Introduction 4
- 1.2 Systems of Units 4
- 1.3 Charge and Current 6
- 1.4 Voltage 9
- 1.5 Power and Energy 10
- 1.6 Circuit Elements 15
- 1.7 †Applications 17
 - 1.7.1 TV Picture Tube
 - 1.7.2 Electricity Bills
- 1.8 †Problem Solving 20
- 1.9 Summary 23
 - Review Questions 24
 - Problems 24
 - Comprehensive Problems 27

Chapter 2 Basic Laws 29

- 2.1 Introduction 30
- 2.2 Ohm's Law 30
- 2.3 †Nodes, Branches, and Loops 35
- 2.4 Kirchhoff's Laws 37
- 2.5 Series Resistors and Voltage Division 43
- 2.6 Parallel Resistors and Current Division 45
- 2.7 †Wye-Delta Transformations 52
- 2.8 †Applications 58
 - 2.8.1 Lighting Systems
 - 2.8.2 Design of DC Meters
- 2.9 Summary 64
 - Review Questions 66

Problems 67

Comprehensive Problems 78

Chapter 3 Methods of Analysis 81

- 3.1 Introduction 82
- 3.2 Nodal Analysis 82
- 3.3 Nodal Analysis with Voltage Sources 88
- 3.4 Mesh Analysis 93
- 3.5 Mesh Analysis with Current Sources 98
- 3.6 †Nodal and Mesh Analyses by Inspection 100
- 3.7 Nodal Versus Mesh Analysis 104
- 3.8 Circuit Analysis with *PSpice* 105
- 3.9 †Applications: DC Transistor Circuits 107
- 3.10 Summary 112
 - Review Questions 113
 - Problems 114
 - Comprehensive Problems 126

Chapter 4 Circuit Theorems 127

- 4.1 Introduction 128
- 4.2 Linearity Property 128
- 4.3 Superposition 130
- 4.4 Source Transformation 135
- 4.5 Thevenin's Theorem 139
- 4.6 Norton's Theorem 145
- 4.7 †Derivations of Thevenin's and Norton's Theorems 149
- 4.8 Maximum Power Transfer 150
- 4.9 Verifying Circuit Theorems with *PSpice* 152
- 4.10 †Applications 155
 - 4.10.1 Source Modeling
 - 4.10.2 Resistance Measurement
- 4.11 Summary 160
 - Review Questions 161
 - Problems 162
 - Comprehensive Problems 173

Chapter 5	Operational Amplifiers	175	7.8	Transient Analysis with <i>PSpice</i>	289
5.1	Introduction	176	7.9	†Applications	293
5.2	Operational Amplifiers	176	7.9.1	Delay Circuits	
5.3	Ideal Op Amp	179	7.9.2	Photoflash Unit	
5.4	Inverting Amplifier	181	7.9.3	Relay Circuits	
5.5	Noninverting Amplifier	183	7.9.4	Automobile Ignition Circuit	
5.6	Summing Amplifier	185	7.10	Summary	299
5.7	Difference Amplifier	187		Review Questions	300
5.8	Cascaded Op Amp Circuits	191		Problems	301
5.9	Op Amp Circuit Analysis with <i>PSpice</i>	194		Comprehensive Problems	311
5.10	†Applications	196	Chapter 8	Second-Order Circuits	313
5.10.1	Digital-to-Analog Converter		8.1	Introduction	314
5.10.2	Instrumentation Amplifiers		8.2	Finding Initial and Final Values	314
5.11	Summary	199	8.3	The Source-Free Series <i>RLC</i> Circuit	319
	Review Questions	201	8.4	The Source-Free Parallel <i>RLC</i> Circuit	326
	Problems	202	8.5	Step Response of a Series <i>RLC</i> Circuit	331
	Comprehensive Problems	213	8.6	Step Response of a Parallel <i>RLC</i> Circuit	336
Chapter 6	Capacitors and Inductors	215	8.7	General Second-Order Circuits	339
6.1	Introduction	216	8.8	Second-Order Op Amp Circuits	344
6.2	Capacitors	216	8.9	<i>PSpice</i> Analysis of <i>RLC</i> Circuits	346
6.3	Series and Parallel Capacitors	222	8.10	†Duality	350
6.4	Inductors	226	8.11	†Applications	353
6.5	Series and Parallel Inductors	230	8.11.1	Automobile Ignition System	
6.6	†Applications	233	8.11.2	Smoothing Circuits	
6.6.1	Integrator		8.12	Summary	356
6.6.2	Differentiator			Review Questions	357
6.6.3	Analog Computer			Problems	358
6.7	Summary	240		Comprehensive Problems	367
	Review Questions	241	PART 2	AC Circuits	368
	Problems	242	Chapter 9	Sinusoids and Phasors	369
	Comprehensive Problems	251	9.1	Introduction	370
Chapter 7	First-Order Circuits	253	9.2	Sinusoids	371
7.1	Introduction	254	9.3	Phasors	376
7.2	The Source-Free <i>RC</i> Circuit	254	9.4	Phasor Relationships for Circuit Elements	385
7.3	The Source-Free <i>RL</i> Circuit	259			
7.4	Singularity Functions	265			
7.5	Step Response of an <i>RC</i> Circuit	273			
7.6	Step Response of an <i>RL</i> Circuit	280			
7.7	†First-Order Op Amp Circuits	284			

- 9.5 Impedance and Admittance 387
- 9.6 †Kirchhoff's Laws in the Frequency Domain 389
- 9.7 Impedance Combinations 390
- 9.8 †Applications 396
 - 9.8.1 Phase-Shifters
 - 9.8.2 AC Bridges
- 9.9 Summary 402
 - Review Questions 403
 - Problems 403
 - Comprehensive Problems 411

Chapter 10 Sinusoidal Steady-State Analysis 413

- 10.1 Introduction 414
- 10.2 Nodal Analysis 414
- 10.3 Mesh Analysis 417
- 10.4 Superposition Theorem 421
- 10.5 Source Transformation 424
- 10.6 Thevenin and Norton Equivalent Circuits 426
- 10.7 Op amp AC Circuits 431
- 10.8 AC Analysis Using *PSpice* 433
- 10.9 †Applications 437
 - 10.9.1 Capacitance Multiplier
 - 10.9.2 Oscillators
- 10.10 Summary 441
 - Review Questions 441
 - Problems 443

Chapter 11 AC Power Analysis 457

- 11.1 Introduction 458
- 11.2 Instantaneous and Average Power 458
- 11.3 Maximum Average Power Transfer 464
- 11.4 Effective or RMS Value 467
- 11.5 Apparent Power and Power Factor 470
- 11.6 Complex Power 473
- 11.7 †Conservation of AC Power 477
- 11.8 Power Factor Correction 481
- 11.9 †Applications 483

- 11.9.1 Power Measurement
- 11.9.2 Electricity Consumption Cost
- 11.10 Summary 488
 - Review Questions 490
 - Problems 490
 - Comprehensive Problems 500

Chapter 12 Three-Phase Circuits 503

- 12.1 Introduction 504
- 12.2 Balanced Three-Phase Voltages 505
- 12.3 Balanced Wye-Wye Connection 509
- 12.4 Balanced Wye-Delta Connection 512
- 12.5 Balanced Delta-Delta Connection 514
- 12.6 Balanced Delta-Wye Connection 516
- 12.7 Power in a Balanced System 519
- 12.8 †Unbalanced Three-Phase Systems 525
- 12.9 *PSpice* for Three-Phase Circuits 529
- 12.10 †Applications 534
 - 12.10.1 Three-Phase Power Measurement
 - 12.10.2 Residential Wiring
- 12.11 Summary 543
 - Review Questions 543
 - Problems 544
 - Comprehensive Problems 553

Chapter 13 Magnetically Coupled Circuits 555

- 13.1 Introduction 556
- 13.2 Mutual Inductance 557
- 13.3 Energy in a Coupled Circuit 564
- 13.4 Linear Transformers 567
- 13.5 Ideal Transformers 573
- 13.6 Ideal Autotransformers 581
- 13.7 †Three-Phase Transformers 584
- 13.8 *PSpice* Analysis of Magnetically Coupled Circuits 586
- 13.9 †Applications 591
 - 13.9.1 Transformer as an Isolation Device
 - 13.9.2 Transformer as a Matching Device
 - 13.9.3 Power Distribution
- 13.10 Summary 597

Review Questions	598
Problems	599
Comprehensive Problems	611
Chapter 14	Frequency Response 613
14.1	Introduction 614
14.2	Transfer Function 614
14.3	†The Decibel Scale 617
14.4	Bode Plots 619
14.5	Series Resonance 629
14.6	Parallel Resonance 634
14.7	Passive Filters 637
14.7.1	Lowpass Filter
14.7.2	Highpass Filter
14.7.3	Bandpass Filter
14.7.4	Bandstop Filter
14.8	Active Filters 642
14.8.1	First-Order Lowpass Filter
14.8.2	First-Order Highpass Filter
14.8.3	Bandpass Filter
14.8.4	Bandreject (or Notch) Filter
14.9	†Scaling 648
14.9.1	Magnitude Scaling
14.9.2	Frequency Scaling
14.9.3	Magnitude and Frequency Scaling
14.10	Frequency Response Using <i>PSpice</i> 652
14.11	Computation Using <i>MATLAB</i> 655
14.12	†Applications 657
14.12.1	Radio Receiver
14.12.2	Touch-Tone Telephone
14.12.3	Crossover Network
14.12	Summary 663
	Review Questions 664
	Problems 665
	Comprehensive Problems 673
PART 3	Advanced Circuit Analysis 674
Chapter 15	Introduction to the Laplace Transform 675
15.1	Introduction 676
15.2	Definition of the Laplace Transform 677
15.3	Properties of the Laplace Transform 679
15.4	The Inverse Laplace Transform 690
15.4.1	Simple Poles
15.4.2	Repeated Poles
15.4.3	Complex Poles
15.5	The Convolution Integral 697
15.6	†Application to Integrodifferential Equations 705
15.7	Summary 708
	Review Questions 708
	Problems 709
Chapter 16	Applications of the Laplace Transform 715
16.1	Introduction 716
16.2	Circuit Element Models 716
16.3	Circuit Analysis 722
16.4	Transfer Functions 726
16.5	State Variables 730
16.6	†Applications 737
16.6.1	Network Stability
16.6.2	Network Synthesis
16.7	Summary 745
	Review Questions 746
	Problems 747
	Comprehensive Problems 754
Chapter 17	The Fourier Series 755
17.1	Introduction 756
17.2	Trigonometric Fourier Series 756
17.3	Symmetry Considerations 764
17.3.1	Even Symmetry
17.3.2	Odd Symmetry
17.3.3	Half-Wave Symmetry
17.4	Circuit Applications 774
17.5	Average Power and RMS Values 778
17.6	Exponential Fourier Series 781
17.7	Fourier Analysis with <i>PSpice</i> 787
17.7.1	Discrete Fourier Transform
17.7.2	Fast Fourier Transform
17.8	†Applications 793
17.8.1	Spectrum Analyzers
17.8.2	Filters

17.9	Summary	796	19.4	Hybrid Parameters	858
	Review Questions	798	19.5	Transmission Parameters	863
	Problems	798	19.6	†Relationships Between Parameters	868
	Comprehensive Problems	807	19.7	Interconnection of Networks	871
Chapter 18 Fourier Transform 809			19.8	Computing Two-Port Parameters Using <i>PSpice</i>	877
18.1	Introduction	810	19.9	†Applications	880
18.2	Definition of the Fourier Transform	810	19.9.1	Transistor Circuits	
18.3	Properties of the Fourier Transform	816	19.9.2	Ladder Network Synthesis	
18.4	Circuit Applications	829	19.10	Summary	889
18.5	Parseval's Theorem	832		Review Questions	890
18.6	Comparing the Fourier and Laplace Transforms	835		Problems	890
18.7	†Applications	836		Comprehensive Problems	901
	18.7.1 Amplitude Modulation		Appendix A	Simultaneous Equations and Matrix Inversion	A
	18.7.2 Sampling		Appendix B	Complex Numbers	A-9
18.8	Summary	839	Appendix C	Mathematical Formulas	A-16
	Review Questions	840	Appendix D	<i>KCIDE for Circuits</i>	A-21
	Problems	841	Appendix E	Answers to Odd-Numbered Problems	A-31
	Comprehensive Problems	847		<i>Selected Bibliography</i>	B-1
Chapter 19 Two-Port Networks 849				<i>Index</i>	I-1
19.1	Introduction	850			
19.2	Impedance Parameters	850			
19.3	Admittance Parameters	855			