

1.1	Introduction	1
1.2	Overview of the Text	2
1.3	Relationship of Circuit Analysis to Engineering	3
1.4	Analysis and Design	4
1.5	Computer-Aided Analysis	5
1.6	Successful Problem-Solving Strategies	5
1.7	Recommended Reading	6

2.1	Introduction	7
2.2	Units and Scales	7
2.3	Charge, Current, Voltage, and Power	9
2.4	Voltage and Current Sources	15
2.5	Ohm's Law	19
2.6		

CEA T1R 7

Capacitors and Inductors 725

- 7.1 Introduction 173
- 7.2 The Capacitor 173
- 7.3 The Inductor 180
- 7.4 Inductance and Capacitance Combinations 188
- 7.5 Consequences of Linearity 192
- 7.6 Simple Op Amp Circuits with Capacitors 194
- 7.7 Duality 196
- 7.8 Modeling Capacitors and Inductors with PSpice® 200
- 7.9 Summary and Review 201
- Exercises 202

CEA T1R 8

RL and RC Circuits 977

- 8.1 Introduction 211
- 8.2 The Source-Free RL Circuit 211
- 8.3 Properties of the Exponential Response 216
- 8.4 The Source-Free RC Circuit 220
- 8.5 A More General Perspective 222
- 8.6 The Unit-Step Function 227
- 8.7 Driven RL Circuits 230
- 8.8 Natural and Forced Response 233
- 8.9 Driven RC Circuits 239
- 8.10 Summary and Review 245
- Exercises 245

CEA T1R 9

RLC Circuit 907

- 9.1 Introduction 261
- 9.2 The Source-Free Parallel Circuit 261
- 9.3 The Overdamped Parallel RLC Circuit 265
- 9.4 Critical Damping 270
- 9.5 The Underdamped Parallel RLC Circuit 274
- 9.6 The Source-Free Series RLC Circuit 280
- 9.7 The Complete Response of the RLC Circuit 284
- 9.8 The Lossless LC Circuit 292
- 9.9 Summary and Review 294
- Exercises 295

CEA T1R 10

Sinusoidal Steady-State Analysis 545

- 10.1 Introduction 303
- 10.2 Characteristics of Sinusoids 303
- 10.3 Forced Response to Sinusoidal Functions 306
- 10.4 The Complex Forcing Function 309
- 10.5 The Phasor 314
- 10.6 Phasor Relationships for R , L , and C 317
- 10.7 Impedance 321
- 10.8 Admittance 326
- 10.9 Nodal and Mesh Analysis 327
- 10.10 Superposition, Source Transformations, and Thévenin's Theorem 331
- 10.11 Phasor Diagrams 336
- 10.12 Summary 340
- Exercises 340

CEA T1R 11

AC Power Circuit Analysis 585

- 11.1 Introduction 353
- 11.2 Instantaneous Power 354
- 11.3 Average Power 356
- 11.4 Effective Values of Current and Voltage 366
- 11.5 Apparent Power and Power Factor 371
- 11.6 Complex Power 373
- 11.7 Comparison of Power Terminology 378
- 11.8 Summary and Review 379
- Exercises 380

CEA T1R 12

Three-Phase Circuits 586

- 12.1 Introduction 389
- 12.2 Polyphase Systems 390
- 12.3 Single-Phase Three-Wire Systems 392
- 12.4 Three-Phase Y-Y Connection 396
- 12.5 The Delta (Δ) Connection 401
- 12.6 Power Measurement in Three-Phase Systems 406
- 12.7 Summary and Review 415
- Exercises 416

CEA T1R 3
Magnetically Coupled Circuits 395

- 131 Introduction 423
 - 132 Mutual Inductance 424
 - 133 Energy Considerations 431
 - 134 The Linear Transformer 434
 - 135 The Ideal Transformer 440
 - 136 Summary and Review 450
- Exercises 450

CEA T1R 4
Complex Frequency and the Laplace Transform 307

- 141 Introduction 461
 - 142 Complex Frequency 461
 - 143 The Damped Sinusoidal Forcing Function 465
 - 144 Definition of the Laplace Transform 468
 - 145 Laplace Transforms of Simple Time Functions 471
 - 146 Inverse Transform Techniques 474
 - 147 Basic Theorems for the Laplace Transform 479
 - 148 The Initial-Value and Final-Value Theorems 485
 - 149 Summary and Review 488
- Exercises 488

CEA T1R 5
Circuit Analysis in the s -Plane 368

- 151 Introduction 495
 - 152 $Z(s)$ and $Y(s)$ 495
 - 153 Nodal and Mesh Analysis in the s -Domain 501
 - 154 Additional Circuit Analysis Techniques 507
 - 155 Poles, Zeros, and Transfer Functions 510
 - 156 Convolution 511
 - 157 The Complex-Frequency Plane 520
 - 158 Natural Response and the s -Plane 529
 - 159 A Technique for Synthesizing the Voltage Ratio $H(s) = V_{out}/V_{in}$ 534
 - 1510 Summary and Review 536
- Exercises 537

CEA T1R 6
Frequency Response 838

- 161 Introduction 545
 - 162 Parallel Resonance 545
 - 163 More about Parallel Resonance 553
 - 164 Series Resonance 559
 - 165 Other Resonant Forms 561
 - 166 Scaling 569
 - 167 Bode Diagrams 574
 - 168 Filters 587
 - 169 Summary and Review 595
- Exercises 596

CEA T1R 7
Two-Port Networks 048

- 171 Introduction 605
 - 172 One-Port Networks 605
 - 173 Admittance Parameters 610
 - 174 Some Equivalent Networks 617
 - 175 Impedance Parameters 625
 - 176 Hybrid Parameters 630
 - 177 Transmission Parameters 633
 - 178 Summary and Review 637
- Exercises 637

CEA T1R 8
Fourier Circuit Analysis 038

- 181 Introduction 645
- 182 Trigonometric Form of the Fourier Series 646
- 183 The Use of Symmetry 654
- 184 Complete Response to Periodic Forcing Functions 658
- 185 Complex Form of the Fourier Series 661
- 186 Definition of the Fourier Transform 667
- 187 Some Properties of the Fourier Transform 670
- 188 Fourier Transform Pairs for Some Simple Time Functions 674
- 189 The Fourier Transform of a General Periodic Time Function 678
- 1810 The System Function and Response in the Frequency Domain 680

181 The Physical Significance of the System Function 685

182 Summary and Review 689

Exercises 690

C E A T 1 R 

State Variable Analysis

191 Introduction

192 State Variables and Normal-Form Equations

193 Writing a Set of Normal-Form Equations

194 The Use of Matrix Notation









195 Solution of the First-Order Equation

196 The Solution of the Matrix Equation

197 A Further Look at the State-Transition Matrix

198 Summary and Review

Exercises

	An Introduction to Network Topology	697
	Solution of Simultaneous Equations	709
	A Proof of Thévenin's Theorem	717
	A PSpice® Tutorial	721
	Complex Numbers	727
	A Brief MATLAB® Tutorial	737
	Additional Laplace Transform Theorems	741
	Answers to Odd-Numbered Problems	747

hex 228