

5. The equivalent resistance of two resistors connected in series is found by taking the sum of the two resistances or

$$R_s = R_1 + R_2$$

$$R_s = 20 \Omega + 20 \Omega$$

$$R_s = 40 \Omega$$