

and one negative) instead of one. The DC bias circuit connected to the base consists of a single resistor. Determine V_{CEQ} and the region of operation.

$$\begin{aligned} V_{CC} &= 12 \text{ V} & V_{EE} &= 4 \text{ V} \\ \beta &= 100 & R_B &= 100 \text{ k}\Omega \\ R_C &= 3 \text{ k}\Omega & R_E &= 3 \text{ k}\Omega \\ R_L &= 6 \text{ k}\Omega & R_S &= 0.6 \text{ k}\Omega \\ v_S &= 1 \cos(6.28 \times 10^3 t) \text{ mV} \end{aligned}$$

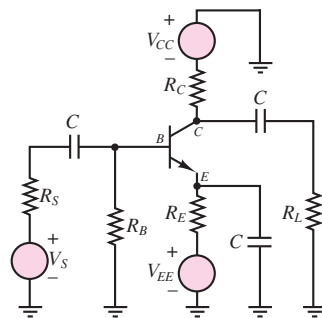


Figure P10.33

10.34 Shown in Figure P10.34 is a common-emitter amplifier stage implemented with an *npn* silicon transistor. The DC bias circuit connected to the base consists of a single resistor; however, it is connected directly between base and collector. Determine V_{CEQ} and the region of operation.

$$\begin{aligned} V_{CC} &= 12 \text{ V} \\ \beta &= 130 & R_B &= 325 \text{ k}\Omega \\ R_C &= 1.9 \text{ k}\Omega & R_E &= 2.3 \text{ k}\Omega \\ R_L &= 10 \text{ k}\Omega & R_S &= 0.5 \text{ k}\Omega \\ v_S &= 1 \cos(6.28 \times 10^3 t) \text{ mV} \end{aligned}$$

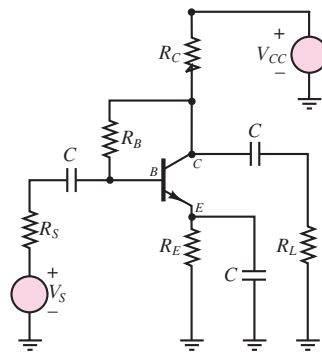


Figure P10.34

10.35 For the circuit shown in Figure P10.35 v_S is a small sine wave signal with average value of 3 V. If $\beta = 100$ and $R_B = 60 \text{ k}\Omega$.

- Find the value of R_E so that I_E is 1 mA.
- Find R_C so that V_C is 5 V.
- For $R_L = 5 \text{ k}\Omega$, find the small-signal equivalent circuit of the amplifier.
- Find the voltage gain.


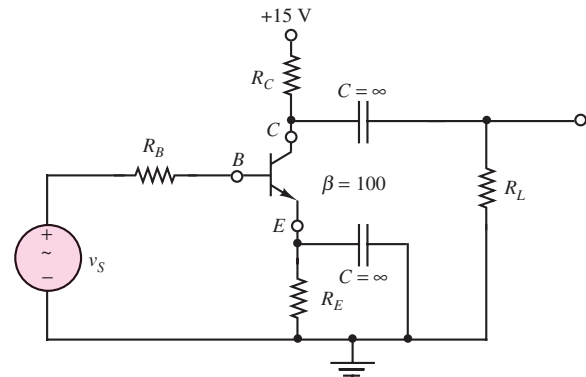


Figure P10.35

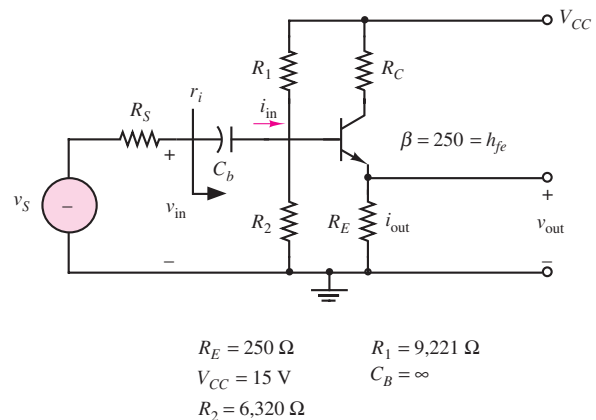10.36 The circuit in Figure P10.36 is in the common-collector configuration. Assuming $R_C = 200 \Omega$:

- Find the operating point of the transistor.
- If the voltage gain is defined as v_{out}/v_{in} , find the voltage gain. If the current gain is defined as i_{out}/i_{in} , find the current gain.
- Find the input resistance, r_i .
- Find the output resistance, r_o .



$$\begin{aligned} R_E &= 250 \Omega & R_1 &= 9,221 \Omega \\ V_{CC} &= 15 \text{ V} & C_B &= \infty \\ R_2 &= 6,320 \Omega \end{aligned}$$

Figure P10.36

10.37 The circuit that supplies energy to an automobile's fuel injector is shown in Figure P10.37(a). The internal circuitry of the injector can be