

Figure P11.21

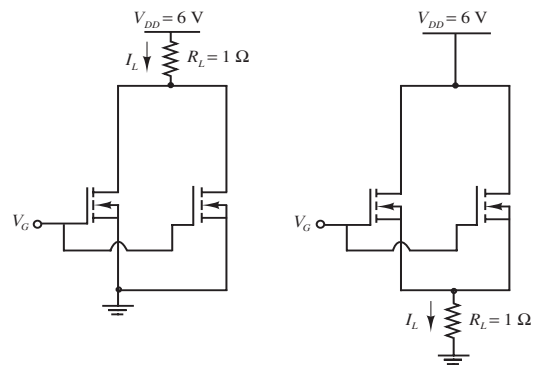


Figure P11.23

- 11.22** A precision voltage source can be created by driving the drain of a MOSFET. Figure P11.22 shows a circuit that will accomplish this function. With $I_{Ref} = 0.01$ A, determine the output V_G . Let $K = 0.006$ mA/V² and $V_T = 1.5$ V.

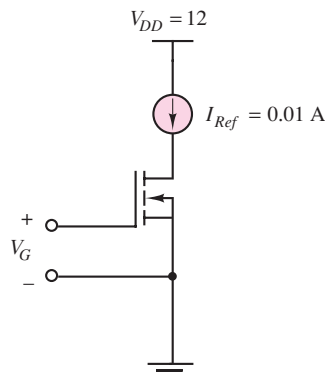


Figure P11.22

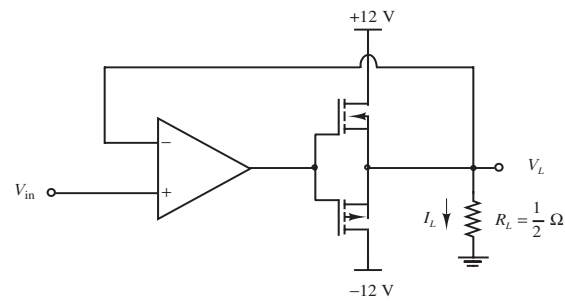


Figure P11.24

- 11.25** Determine the $V - I$ characteristics of the voltage controlled resistance shown in the circuit of Figure P11.25.

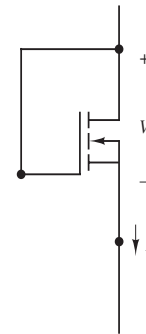


Figure P11.25

- 11.23** To allow more current in a MOSFET amplifier, several MOSFETs can be connected in parallel. Determine the load current in each of the circuits of Figure P11.23. Let $K = 0.2$ A/V² and $V_T = 3$ V.
- 11.24** A “push-pull amplifier” can be constructed from matched n - and p -channel MOSFETs, as shown in Figure P11.24. Let $K_n = K_p = 0.5$ A/V², $V_{Tn} = +3$ V, $V_{Tp} = -3$ V and $V_{in} = 0.8 \cos(1,000t)$ V. Determine V_L and I_L .

- 11.26** Determine V_L and I_L for the two-stage amplifier shown in the circuit of Figure P11.26, with identical MOSFETs having $K = 1$ A/V² and $V_T = 3$ V, for
- $V_G = 4$ V,
 - $V_G = 5$ V, and
 - $V_G = 4 + 0.1 \cos(750t)$.