

Figure P12.2

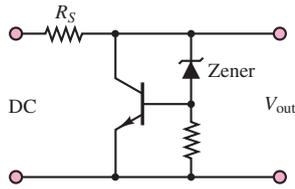


Figure P12.3

Section 12.4: Power Amplifiers

12.4 The circuit of Figure P12.4 is a very effective battery charger. Its operation is simple, and the TIP-33C *n-p-n* power transistor can sink 40 A amps if a big enough heat sink is used. Assuming that the transistor is in the linear operating region, determine the power delivered to the 1.2 V rechargeable battery in the circuit.

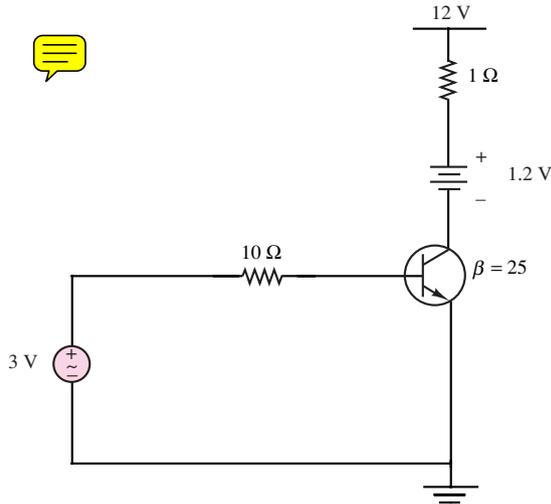


Figure P12.4

12.5 An IGBT can be modeled as shown in the circuit of Figure P12.5. With $V_T = 4$ and $K = 0.01 \text{ A/V}^2$ for MOSFET, and $\beta = 200$ for the BJT, determine the current through R_L and the voltage across it. Let $V_G = 8 \text{ V}$.

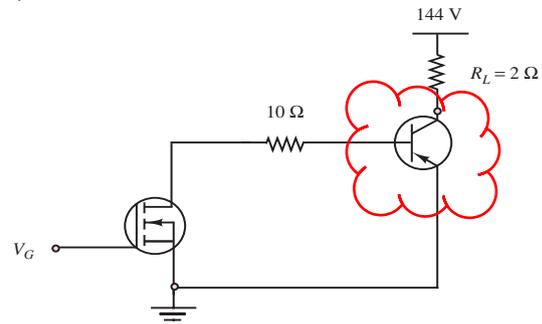


Figure P12.5

Section 12.5: Rectifiers and Controlled Rectifiers (AC-DC Converters)

12.6 For the circuit shown in Figure 12.19 in the text, if the *LR* load is replaced by a capacitor, draw the output waveform and label the values.

12.7 Draw $v_L(t)$ and label the values for the circuit in Figure 12.19 in the text if the diode forward resistance is 50Ω , the forward bias voltage is 0.7 V , and the load consists of a resistor $R = 10 \Omega$ and an inductor $L = 2 \text{ H}$.

12.8 For the circuit shown in Figure P12.8, v_{AC} is a sinusoid with 10-V peak amplitude, $R = 2 \text{ k}\Omega$, and the forward-conducting voltage of D is 0.7 V .

- a. Sketch the waveform of $v_L(t)$.
- b. Find the average value of $v_L(t)$.

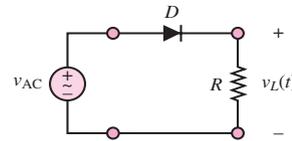


Figure P12.8

12.9 A vehicle battery charge circuit is shown in Figure P12.9. Describe the circuit, and draw the output waveform (L_1 and L_2 represent the inductances of the windings of the alternator).

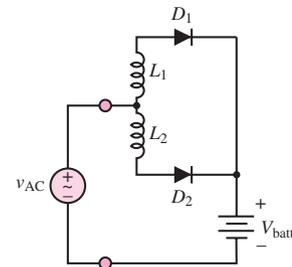


Figure P12.9