

Figure P12.18

12.19 A power supply is shown in Figure P12.19. Sketch the signals V_{ab} , V_{cd} , V_{ef} , and I_Z .

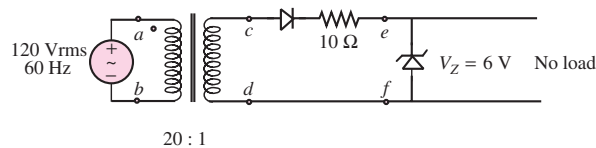


Figure P12.19

12.20 Figure P12.20 depicts a low-cost full-wave rectifier with a Zener diode voltage regulator. Sketch the voltages across terminals a - b , c - d , and e - f .

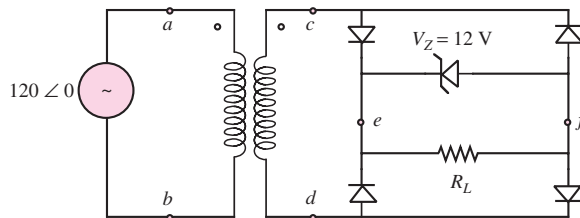


Figure P12.20

12.21 In the DC power supply shown in Figure P12.21, sketch the voltage across a - b , c - a , and d - e , assuming that R is so large as to make any ripple not noticeable.

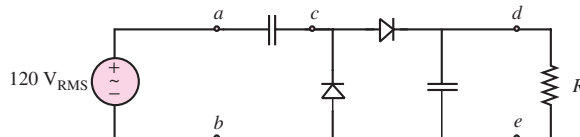


Figure P12.21

12.22 A DC power supply known as a *voltage doubler* is shown in Figure P12.22. It is assumed that the capacitors are large enough that the ripple is not

significant in the output voltage. Sketch the signals V_{ab} and V_{cd} . Assume the input is at 60 Hz.

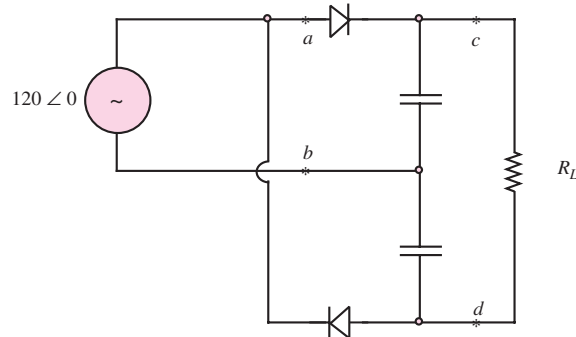


Figure P12.22

Section 12.6: Electric Motor Drives

12.23 The DC-DC converter of Figure 12.37 in the text, is used to control the speed of a DC motor. Let the supply voltage be 120 V and the armature resistance of the motor be 0.15Ω . The motor back-emf constant is 0.05 V/(r/min) , and the switching frequency is 250 Hz. Assume that the motor current is free of ripple and equal to 125 A at 120 r/min.

- Determine the duty cycle of the converter, δ and the converter on time t_1 .
- Determine the power absorbed by the motor.
- Determine the power generated by the supply.

12.24 The circuit of Figure 12.41 in the text, is used to provide regenerative braking in a traction motor. The motor constant is 0.3 V/(r/min) , and the supply voltage is 600 V. The armature resistance is $R_a = 0.2 \Omega$. The motor speed is 800 r/min and the motor current is 300 A.

- Determine the duty cycle δ of the converter.
- Determine the power fed back to the supply (battery).

12.25 For the two-quadrant converter of Figure 12.42 in the text, assume that thyristors S_1 and S_2 are turned on for time t_1 and off for time $T - t_1$ (T is the switching period). Derive an expression for the average output voltage in terms of the supply voltage V_S and the duty cycle δ .

12.26 A boost converter is powered by an ideal 100-V battery pack. The load voltage waveform consists of rectangular pulses with on time = 1 ms and period equal to 2.5 ms. Calculate the average and rms values of the converter supply voltage.

12.27 A buck converter connected to a 100-V battery pack supplies an RL load with $R = 0.5 \Omega$ and $L =$