

- 2.49** For the circuit shown in Figure P2.49, find the equivalent resistance, where  $R_1 = 5\ \Omega$ ,  $R_2 = 1\ \text{k}\Omega$ ,  $R_3 = R_4 = 100\ \Omega$ ,  $R_5 = 9.1\ \Omega$  and  $R_6 = 1\ \text{k}\Omega$ .

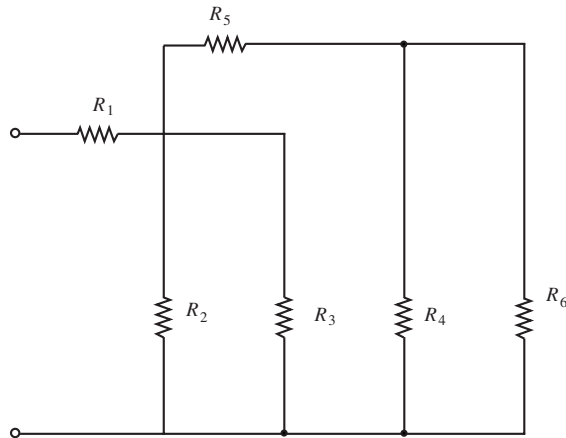


Figure P2.49

- 2.50** Cheap resistors are fabricated by depositing a thin layer of carbon onto a nonconducting cylindrical substrate (see Figure P2.50). If such a cylinder has radius  $a$  and length  $d$ , determine the thickness of the film required for a resistance  $R$  if

$$a = 1\ \text{mm} \quad R = 33\ \text{k}\Omega$$

$$\sigma = \frac{1}{\rho} = 2.9\ \text{M}\frac{\text{S}}{\text{m}} \quad d = 9\ \text{mm}$$

Neglect the end surfaces of the cylinder and assume that the thickness is much smaller than the radius.

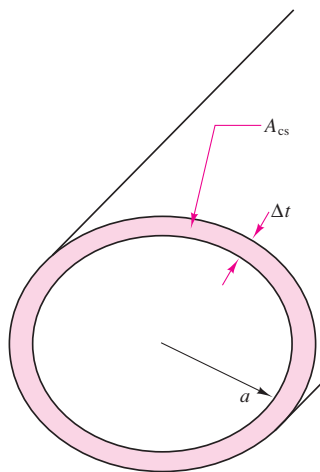


Figure P2.50

- 2.51** The resistive elements of fuses, lightbulbs, heaters, etc., are significantly nonlinear (i.e., the resistance is dependent on the current through the element).

Assume the resistance of a fuse (Figure P2.51) is given by the expression  $R = R_0[1 + A(T - T_0)]$  with  $T - T_0 = kP$ ;  $T_0 = 25^\circ\text{C}$ ;  $A = 0.7[^\circ\text{C}]^{-1}$ ;  $k = 0.35^\circ\text{C}/\text{W}$ ;  $R_0 = 0.11\ \Omega$ ; and  $P$  is the power dissipated in the resistive element of the fuse. Determine the rated current at which the circuit will melt and open, that is, “blow” (Hint: The fuse blows when  $R$  becomes infinite.)

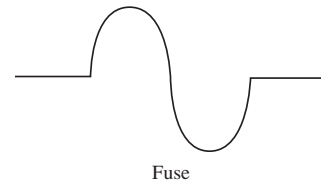


Figure P2.51

- 2.52** Use Kirchhoff's current law and Ohm's law to determine the current in each of the resistors  $R_4$ ,  $R_5$ , and  $R_6$  in the circuit of Figure P2.52.  $V_S = 10\ \text{V}$ ,  $R_1 = 20\ \Omega$ ,  $R_2 = 40\ \Omega$ ,  $R_3 = 10\ \Omega$ ,  $R_4 = R_5 = R_6 = 15\ \Omega$ .

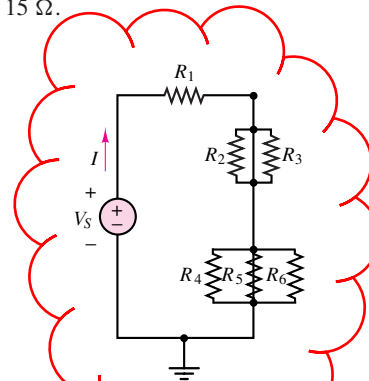


Figure P2.52

- 2.53** With reference to Problem 2.13, use Kirchhoff's current law and Ohm's law to find the resistances  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ , and  $R_5$  if  $R_0 = 2\ \Omega$ . Assume  $R_4 = \frac{2}{3}R_1$  and  $R_2 = \frac{1}{3}R_1$ .
- 2.54** Assuming  $R_1 = 2\ \Omega$ ,  $R_2 = 5\ \Omega$ ,  $R_3 = 4\ \Omega$ ,  $R_4 = 1\ \Omega$ ,  $R_5 = 3\ \Omega$ ,  $I_2 = 4\ \text{A}$ , and  $V_S = 54\ \text{V}$  in the circuit of Figure P2.13, use Kirchhoff's current law and Ohm's law to find
- $I_0$ ,  $I_1$ ,  $I_3$ , and  $I_S$ .
  - $R_0$ .
- 2.55** Assuming  $R_0 = 2\ \Omega$ ,  $R_1 = 1\ \Omega$ ,  $R_2 = 4/3\ \Omega$ ,  $R_3 = 6\ \Omega$ , and  $V_S = 12\ \text{V}$  in the circuit of Figure P2.55, use Kirchhoff's voltage law and Ohm's law to find
- $i_a$ ,  $i_b$ , and  $i_c$ .
  - The current through each resistance.