

Figure P3.15

- 3.16** Using mesh current analysis, find the voltage, v , across the 3-Ω resistor in the circuit of Figure P3.16.

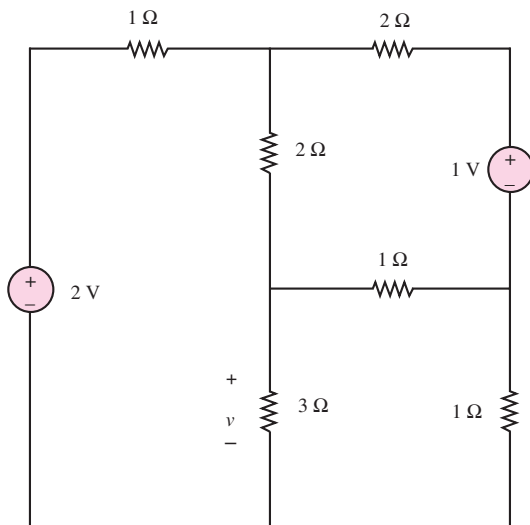


Figure P3.16

- 3.17** Using mesh current analysis, find the currents I_1 , I_2 , and I_3 and the voltage across the 40-Ω resistor in

the circuit of Figure P3.17 (assume polarity according to I_2).

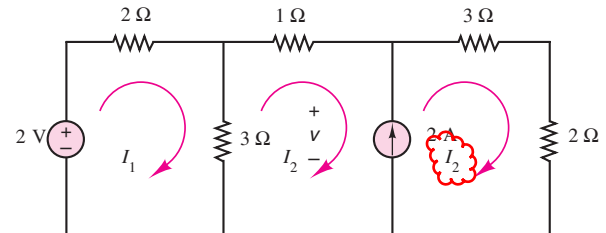


Figure P3.17

- 3.18** Using mesh current analysis, find the voltage, v , across the source in the circuit of Figure P3.18.

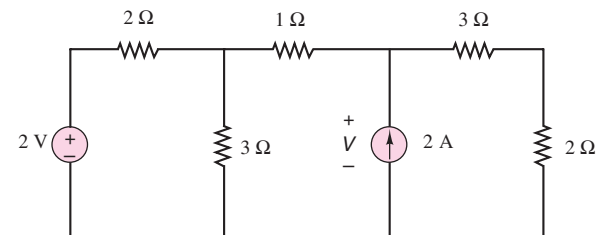


Figure P3.18

- 3.19** a. For the circuit of Figure P3.19, write the mesh equations in matrix form. Notice the form of the $[R]$ and $[V]$ matrices in the $[R][I] = [V]$, where

$$[R] = \begin{bmatrix} r_{11} & r_{12} & r_{13} & \cdots & r_{1n} \\ r_{21} & r_{22} & \cdots & \cdots & r_{2n} \\ r_{31} & & \ddots & & \\ \vdots & & & \ddots & \\ r_{n1} & r_{n2} & \cdots & \cdots & r_{nn} \end{bmatrix} \quad \text{and} \quad [V] = \begin{bmatrix} V_1 \\ V_2 \\ \vdots \\ V_n \end{bmatrix}$$

- b. Write the matrix form of the mesh equations again by using the following formulas:

$$r_{ii} = \sum \text{resistances around loop } i$$

$$r_{ij} = -\sum \text{resistances shared by loops } i \text{ and } j$$

$$V_i = \sum \text{source voltages around loop } i$$