

Figure P3.57

**3.58** Find the Thévenin equivalent of the circuit connected to  $R_L$  in Figure P3.58, where  $R_1 = 10\ \Omega$ ,  $R_2 = 20\ \Omega$ ,  $R_g = 0.1\ \Omega$ , and  $R_p = 1\ \Omega$ .

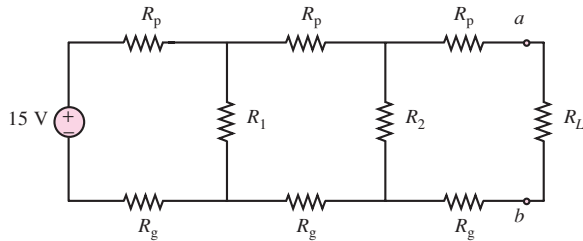


Figure P3.58

**3.59** The Wheatstone bridge circuit shown in Figure P3.59 is used in a number of practical applications. One traditional use is in determining the value of an unknown resistor  $R_x$ . Find the value of the voltage  $V_{ab} = V_a - V_b$  in terms of  $R$ ,  $R_x$ , and  $V_S$ . If  $R = 1\ \text{k}\Omega$ ,  $V_S = 12\ \text{V}$  and  $V_{ab} = 12\ \text{mV}$ , what is the value of  $R_x$ ?

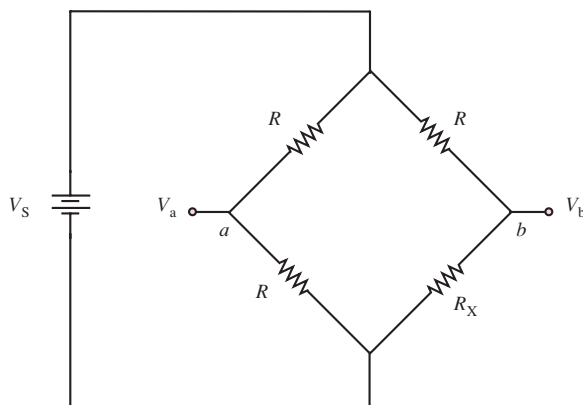


Figure P3.59

**3.60** It is sometimes useful to compute a Thévenin equivalent circuit for a Wheatstone bridge. For the circuit of Figure P3.60,

- Find the Thévenin equivalent resistance seen by the load resistor  $R_L$ .
- If  $V_S = 12\ \text{V}$ ,  $R_1 = R_2 = R_3 = 1\ \text{k}\Omega$ , and  $R_x$  is the resistance found in part b of the previous problem, use the Thévenin equivalent to compute the power dissipated by  $R_L$ , if  $R_L = 500\ \Omega$ .
- Find the power dissipated by the Thévenin equivalent resistance  $R_T$  with  $R_L$  included in the circuit.
- Find the power dissipated by the bridge without the load resistor in the circuit.

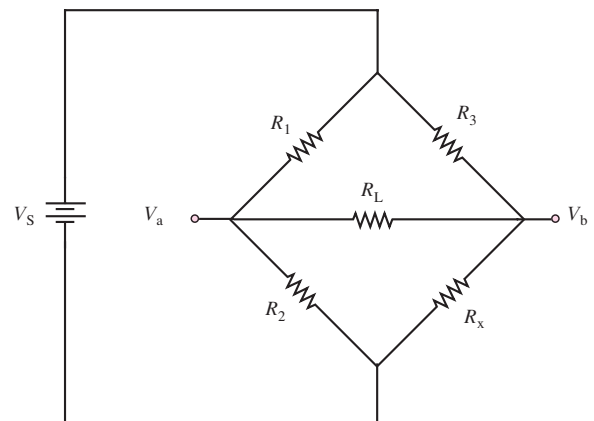


Figure P3.60

**3.61** The circuit shown in Figure P3.61 is in the form of what is known as a *differential amplifier*. Find the expression for  $v_0$  in terms of  $v_1$  and  $v_2$  using Thévenin's or Norton's theorem.

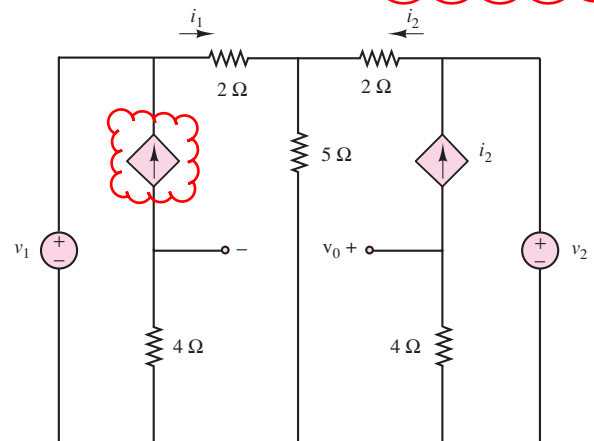


Figure P3.61

**3.62** Find the Thévenin equivalent resistance seen by resistor  $R_3$  in the circuit of Figure P3.5. Compute the