

Figure P3.19

**3.20** For the circuit of Figure P3.20, use mesh current analysis to find the matrices required to solve the circuit, and solve for the unknown currents. [Hint: you may find source transformations useful.]

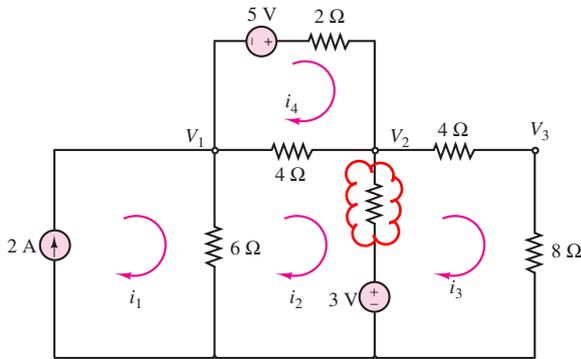


Figure P3.20

**3.21** In the circuit in Figure P3.21, assume the source voltage and source current and all resistances are known.

- Write the node equations required to determine the node voltages.
- Write the matrix solution for each node voltage in terms of the known parameters.

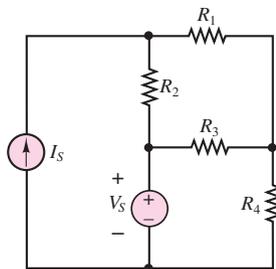


Figure P3.21

**3.22** For the circuit of Figure P3.22 determine

- The most efficient way to solve for the voltage across  $R_3$ . Prove your case.
- The voltage across  $R_3$ .

$$V_{S1} = V_{S2} = 110 \text{ V}$$

$$R_1 = 500 \text{ m}\Omega \quad R_2 = 167 \text{ m}\Omega$$

$$R_3 = 700 \text{ m}\Omega$$

$$R_4 = 200 \text{ m}\Omega \quad R_5 = 333 \text{ m}\Omega$$

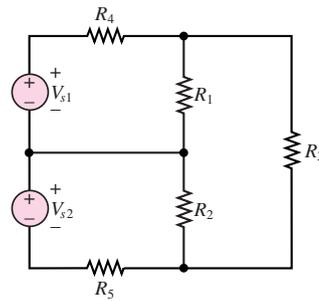


Figure P3.22

**3.23** In the circuit shown in Figure P3.23,  $V_{S2}$  and  $R_s$  model a temperature sensor, i.e.,

$$V_{S2} = kT \quad k = 10 \text{ V}/^\circ\text{C}$$

$$V_{S1} = 24 \text{ V} \quad R_s = R_1 = 12 \text{ k}\Omega$$

$$R_2 = 3 \text{ k}\Omega \quad R_3 = 10 \text{ k}\Omega$$

$$R_4 = 24 \text{ k}\Omega \quad V_{R3} = -2.524 \text{ V}$$

The voltage across  $R_3$ , which is given, indicates the temperature. Determine the temperature.

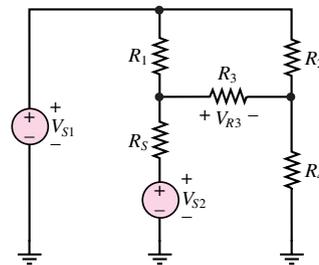


Figure P3.23

**3.24** Using KCL, perform node analysis on the circuit shown in Figure P3.24, and determine the voltage across  $R_4$ . Note that one source is a controlled voltage source! Let  $V_S = 5 \text{ V}$ ;  $A_V = 70$ ;  $R_1 = 2.2 \text{ k}\Omega$ ;  $R_2 = 1.8 \text{ k}\Omega$ ;  $R_3 = 6.8 \text{ k}\Omega$ ;  $R_4 = 220 \Omega$ .