

From these values of Q we can calculate the approximate bandwidth of the two filters:

$$B_a = \frac{\omega_n}{Q_a} \approx 10,000 \text{ rad/s} \quad \text{case a}$$

$$B_b = \frac{\omega_n}{Q_b} \approx 100 \text{ rad/s} \quad \text{case b}$$

The frequency response plots in Figures 6.28 and 6.29 confirm these observations.

Comments: It should be apparent that while at the higher and lower frequencies most of the amplitude of the input signal is filtered from the output, at the midband frequency (4,500 rad/s) most of the input signal amplitude passes through the filter. The first bandpass filter analyzed in this example would “pass” the *midband range* of the audio spectrum, while the second would pass only a very narrow band of frequencies around the **center frequency** of 4,500 rad/s. Such narrowband filters find application in **tuning circuits**, such as those employed in conventional AM radios (although at frequencies much higher than that of the present example). In a tuning circuit, a narrowband filter is used to tune in a frequency associated with the **carrier** of a radio station (e.g., for a station found at a setting of AM 820, the carrier wave transmitted by the radio station is at a frequency of 820 kHz). By using a variable capacitor, it is possible to tune in a range of carrier frequencies and therefore select the preferred station. Other circuits are then used to decode the actual speech or music signal modulated on the carrier wave; some of these are discussed in Chapters 9 and 19.

CHECK YOUR UNDERSTANDING

Compute the frequencies ω_1 and ω_2 for the bandpass filter of Example 6.11 (with $R = 1 \text{ k}\Omega$) for equating the magnitude of the bandpass filter frequency response to $1/\sqrt{2}$ (this will result in a quadratic equation in ω , which can be solved for the two frequencies). Note that these are the **half-power frequencies**.


Answer: $\omega_1 = 99.95 \text{ rad/s}$; $\omega_2 = 200.1 \text{ krad/s}$

Wheatstone Bridge Filter



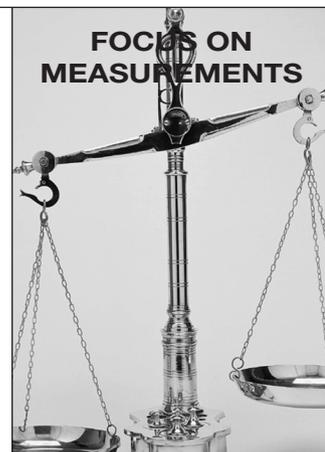Problem:

The Wheatstone bridge circuit of Example 2.14 and Focus on Measurements, “Wheatstone Bridge and Force Measurements” in Chapter 2 is used in a number of instrumentation applications, including the **measurement of force**. Figure 6.30 depicts the appearance of the bridge circuit. When undesired noise and interference are present in a measurement, it is often appropriate to use a low-pass filter to reduce the effect of the noise. The capacitor that is connected to the output terminals of the bridge in Figure 6.30 constitutes an effective and simple low-pass filter, in conjunction with the bridge resistance. Assume that the average resistance of each leg of the bridge is 350Ω (a standard value for strain gauges) and that we desire to measure a sinusoidal



(Continued)