

decreased by the same factor, relative to the maximum value (at the resonant frequency). Since power in an electric signal is proportional to the square of the voltage or current, a drop by a factor  $1/\sqrt{2}$  in the output voltage or current corresponds to the power being reduced by a factor of  $\frac{1}{2}$ . Thus, we term the frequencies at which the intersection of the 0.707 line with the frequency response occurs the **half-power frequencies**. Another useful definition of bandwidth  $B$  is as follows. We shall make use of this definition in the following examples. Note that a high- $Q$  filter has a narrow bandwidth, and a low- $Q$  filter has a wide bandwidth.

$$B = \frac{\omega_n}{Q} \quad \text{bandwidth}$$

(6.46)



### EXAMPLE 6.11 Frequency Response of Bandpass Filter



#### Problem

Compute the frequency response of the bandpass filter of Figure 6.25 for two sets of component values.

#### Solution

##### Known Quantities:

- (a)  $R = 1 \text{ k}\Omega$ ;  $C = 10 \text{ }\mu\text{F}$ ;  $L = 5 \text{ mH}$ .
- (b)  $R = 10 \text{ }\Omega$ ;  $C = 10 \text{ }\mu\text{F}$ ;  $L = 5 \text{ mH}$ .

**Find:** The frequency response  $H_V(j\omega)$ .

**Assumptions:** None.

**Analysis:** We write the frequency response of the bandpass filter as in equation 6.40:

$$\begin{aligned} H_V(j\omega) &= \frac{\mathbf{V}_o}{\mathbf{V}_i}(j\omega) = \frac{j\omega CR}{1 + j\omega CR + (j\omega)^2 LC} \\ &= \frac{\omega CR}{\sqrt{(1 - \omega^2 LC)^2 + (\omega CR)^2}} \angle \left[ \frac{\pi}{2} - \arctan \left( \frac{\omega CR}{1 - \omega^2 LC} \right) \right] \end{aligned}$$

We can now evaluate the response for two different values of the series resistance. The frequency response plots for case a (large series resistance) are shown in Figure 6.28. Those for case b (small series resistance) are shown in Figure 6.29. Let us calculate some quantities for each case. Since  $L$  and  $C$  are the same in both cases, the *resonant frequency* of the two circuits will be the same:

$$\omega_n = \frac{1}{\sqrt{LC}} = 4.47 \times 10^3 \text{ rad/s}$$

On the other hand, the *quality factor*  $Q$  will be substantially different:

$$\begin{aligned} Q_a &= \frac{1}{\omega_n CR} \approx 2.22 \quad \text{case a} \\ Q_b &= \frac{1}{\omega_n CR} \approx 0.022 \quad \text{case b} \end{aligned}$$