

Figure P8.20

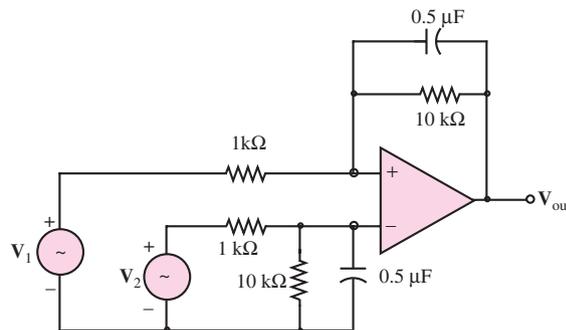


Figure P8.22

**8.21** Differential amplifiers are often used in conjunction with the Wheatstone bridge. Consider the bridge shown in Figure P8.21, where each resistor is a temperature-sensing element and the change in resistance is directly proportional to a change in temperature—that is,  $\Delta R = \alpha (\pm \Delta T)$ , where the sign is determined by the positive or negative temperature coefficient of the resistive element.

- Find the Thévenin equivalent that the amplifier sees at point *a* and point *b*. Assume that  $|\Delta R|^2 \ll R_o$ .
- If  $|\Delta R| = K \Delta T$ , with *K* a numerical constant, find an expression for  $v_{out}(\Delta T)$ , that is  $v_{out}$  as a function of change in temperature.

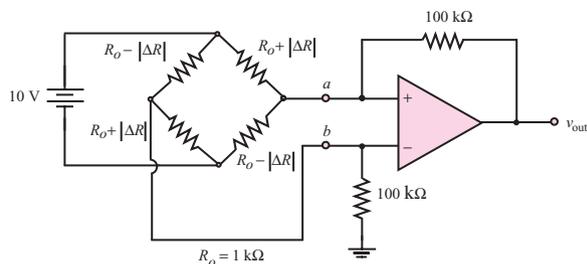


Figure P8.21

**8.22** Consider the circuit of Figure P8.22.

- If  $v_1 - v_2 = \cos(1,000t)$  V, find the peak amplitude of  $v_{out}$ .
- Find the phase shift of  $v_{out}$ .

[Hint: Use phasor analysis.]

**8.23** Find an expression for the gain of the circuit of Figure P8.23.

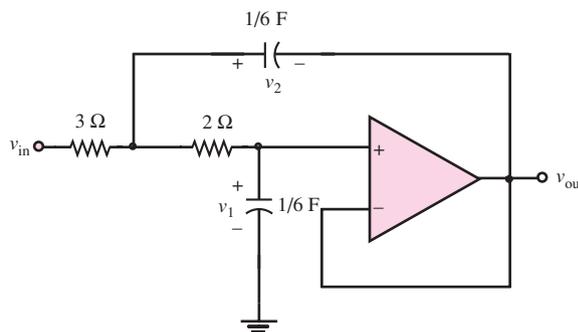


Figure P8.23

**8.24** In the circuit of Figure P8.24, it is critical that the gain remain within 2 percent of its nominal value of 16. Find the resistor  $R_S$  that will accomplish the nominal gain requirement, and state what the maximum and minimum values of  $R_S$  can be. Will a standard 5 percent tolerance resistor be adequate to satisfy this requirement? (See Table 2.1 for resistor standard values.)

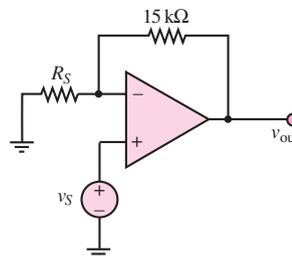


Figure P8.24