

Figure P8.10

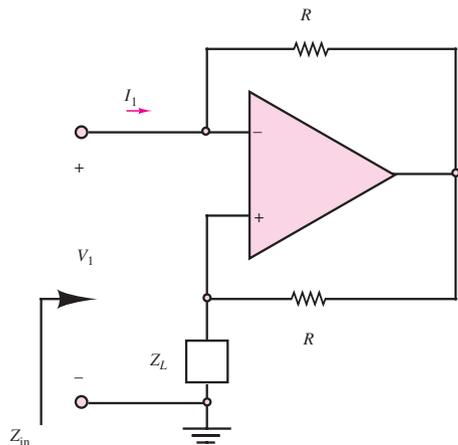


Figure P8.11



8.12 The circuit of Figure P8.12 demonstrates that op-amp feedback can be used to create a resonant circuit without the use of an inductor. Determine the gain function $\frac{V_2}{V_1}$. [Hint: Use node analysis.]

4 Ω

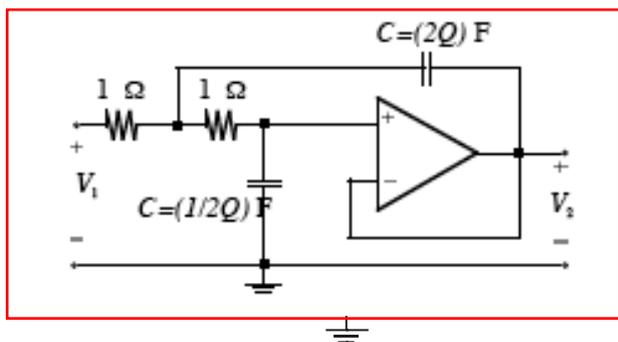


Figure P8.12

8.13 Inductors are difficult to use as components of integrated circuits due to the need for large coils of wire. As an alternative, a “solid-state inductor” can be constructed as in the circuit of Figure 8.13.

- Determine the impedance looking in $Z_{in} = \frac{V_1}{I_1}$.
- What is the impedance when $R = 1,000 \Omega$ and $C = 0.02 \mu\text{F}$?

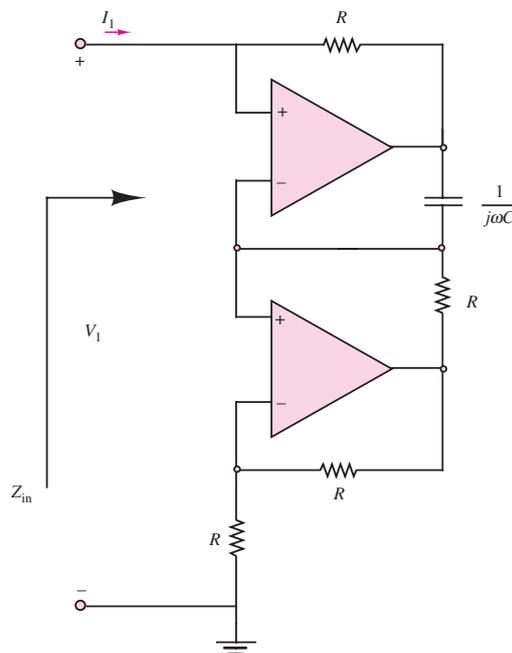


Figure P8.13

8.14 In the circuit of Figure P8.14, determine the impedance looking in.

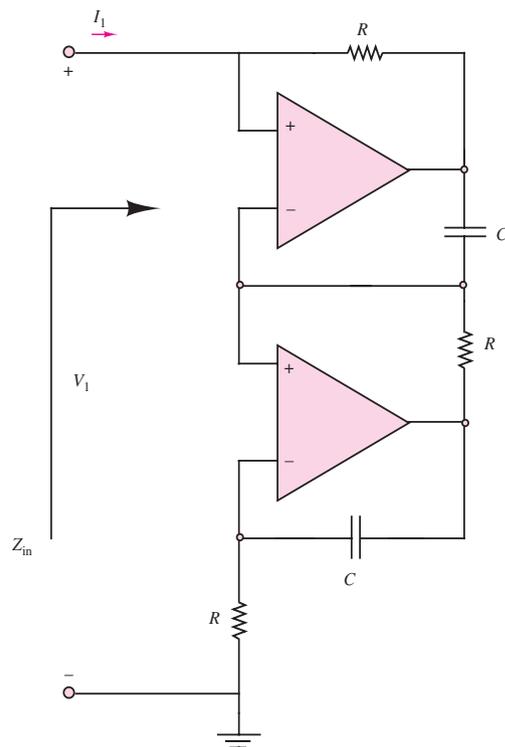


Figure P8.14