

CONTENTS

Lists vii

- Class Discussion Items vii
- Examples ix
- Design Examples x
- Threaded Design Examples xi

Preface xiii

Chapter 1

Introduction 1

- 1.1 Mechatronics 1
- 1.2 Measurement Systems 4
- 1.3 Threaded Design Examples 5

Chapter 2

Electric Circuits and Components 11

- 2.1 Introduction 12
- 2.2 Basic Electrical Elements 14
 - 2.2.1 Resistor 14
 - 2.2.2 Capacitor 19
 - 2.2.3 Inductor 20
- 2.3 Kirchhoff's Laws 22
 - 2.3.1 Series Resistance Circuit 24
 - 2.3.2 Parallel Resistance Circuit 26
- 2.4 Voltage and Current Sources and Meters 30
- 2.5 Thevenin and Norton Equivalent Circuits 35
- 2.6 Alternating Current Circuit Analysis 37
- 2.7 Power in Electrical Circuits 44
- 2.8 Transformer 46

2.9 Impedance Matching 47

2.10 Practical Considerations 50

- 2.10.1 Capacitor Information 50
- 2.10.2 Breadboard and Prototyping Advice 51
- 2.10.3 Voltage and Current Measurement 54
- 2.10.4 Soldering 54
- 2.10.5 The Oscilloscope 58
- 2.10.6 Grounding and Electrical Interference 61
- 2.10.7 Electrical Safety 63

Chapter 3

Semiconductor Electronics 73

3.1 Introduction 74

3.2 Semiconductor Physics as the Basis for Understanding Electronic Devices 74

3.3 Junction Diode 75

- 3.3.1 Zener Diode 81
- 3.3.2 Voltage Regulators 85
- 3.3.3 Optoelectronic Diodes 87
- 3.3.4 Analysis of Diode Circuits 88

3.4 Bipolar Junction Transistor 90

- 3.4.1 Bipolar Transistor Physics 90
- 3.4.2 Common Emitter Transistor Circuit 92
- 3.4.3 Bipolar Transistor Switch 97
- 3.4.4 Bipolar Transistor Packages 99
- 3.4.5 Darlington Transistor 100
- 3.4.6 Phototransistor and Optoisolator 100

3.5 Field-Effect Transistors 102

- 3.5.1 Behavior of Field-Effect Transistors 103
- 3.5.2 Symbols Representing Field-Effect Transistors 106
- 3.5.3 Applications of MOSFETs 107

Chapter 4**System Response** 117

- 4.1 System Response 118
- 4.2 Amplitude Linearity 118
- 4.3 Fourier Series Representation of Signals 120
- 4.4 Bandwidth and Frequency Response 124
- 4.5 Phase Linearity 129
- 4.6 Distortion of Signals 130
- 4.7 Dynamic Characteristics of Systems 131
- 4.8 Zero-Order System 132
- 4.9 First-Order System 134
 - 4.9.1 *Experimental Testing of a First-Order System* 136
- 4.10 Second-Order System 137
 - 4.10.1 *Step Response of a Second-Order System* 141
 - 4.10.2 *Frequency Response of a System* 143
- 4.11 System Modeling and Analogies 150

Chapter 5**Analog Signal Processing Using Operational Amplifiers** 161

- 5.1 Introduction 162
- 5.2 Amplifiers 162
- 5.3 Operational Amplifiers 164
- 5.4 Ideal Model for the Operational Amplifier 164
- 5.5 Inverting Amplifier 167
- 5.6 Noninverting Amplifier 169
- 5.7 Summer 173
- 5.8 Difference Amplifier 173
- 5.9 Instrumentation Amplifier 175
- 5.10 Integrator 177
- 5.11 Differentiator 179
- 5.12 Sample and Hold Circuit 180
- 5.13 Comparator 181
- 5.14 The Real Op Amp 182
 - 5.14.1 *Important Parameters from Op Amp Data Sheets* 183

Chapter 6**Digital Circuits** 197

- 6.1 Introduction 198
- 6.2 Digital Representations 199
- 6.3 Combinational Logic and Logic Classes 202
- 6.4 Timing Diagrams 205
- 6.5 Boolean Algebra 206
- 6.6 Design of Logic Networks 208
 - 6.6.1 *Define the Problem in Words* 208
 - 6.6.2 *Write Quasi-Logic Statements* 209
 - 6.6.3 *Write the Boolean Expression* 209
 - 6.6.4 *And Realization* 210
 - 6.6.5 *Draw the Circuit Diagram* 210
- 6.7 Finding a Boolean Expression Given a Truth Table 211
- 6.8 Sequential Logic 214
- 6.9 Flip-Flops 214
 - 6.9.1 *Triggering of Flip-Flops* 216
 - 6.9.2 *Asynchronous Inputs* 218
 - 6.9.3 *D Flip-Flop* 219
 - 6.9.4 *JK Flip-Flop* 219
- 6.10 Applications of Flip-Flops 222
 - 6.10.1 *Switch Debouncing* 222
 - 6.10.2 *Data Register* 223
 - 6.10.3 *Binary Counter and Frequency Divider* 224
 - 6.10.4 *Serial and Parallel Interfaces* 224
- 6.11 TTL and CMOS Integrated Circuits 226
 - 6.11.1 *Using Manufacturer IC Data Sheets* 228
 - 6.11.2 *Digital IC Output Configurations* 230
 - 6.11.3 *Interfacing TTL and CMOS Devices* 232
- 6.12 Special Purpose Digital Integrated Circuits 235
 - 6.12.1 *Decade Counter* 235
 - 6.12.2 *Schmitt Trigger* 239
 - 6.12.3 *555 Timer* 240
- 6.13 Integrated Circuit System Design 245
 - 6.13.1 *IEEE Standard Digital Symbols* 249

Chapter 7**Microcontroller Programming and Interfacing** 258

- 7.1 Microprocessors and Microcomputers 259
- 7.2 Microcontrollers 261
- 7.3 The PIC16F84 Microcontroller 264
- 7.4 Programming a PIC 268
- 7.5 PicBasic Pro 274
 - 7.5.1 PicBasic Pro Programming Fundamentals 274
 - 7.5.2 PicBasic Pro Programming Examples 282
- 7.6 Using Interrupts 294
- 7.7 Interfacing Common PIC Peripherals 298
 - 7.7.1 Numeric Keypad 298
 - 7.7.2 LCD Display 301
- 7.8 Interfacing to the PIC 306
 - 7.8.1 Digital Input to the PIC 306
 - 7.8.2 Digital Output from the PIC 308
- 7.9 Method to Design a Microcontroller-Based System 309
- 7.10 Practical Considerations 336
 - 7.10.1 PIC Project Debugging Procedure 336
 - 7.10.2 Power Supply Options for PIC Projects 337
 - 7.10.3 Battery Characteristics 339
 - 7.10.4 Other Considerations for Project Prototyping and Design 342

Chapter 8**Data Acquisition** 346

- 8.1 Introduction 347
- 8.2 Quantizing Theory 351
- 8.3 Analog-to-Digital Conversion 352
 - 8.3.1 Introduction 352
 - 8.3.2 Analog-to-Digital Converters 356
- 8.4 Digital-to-Analog Conversion 359
- 8.5 Virtual Instrumentation, Data Acquisition, and Control 363
- 8.6 Practical Considerations 365
 - 8.6.1 Introduction to LabVIEW Programming 365

8.6.2 The USB 6009 Data Acquisition Card 367

8.6.3 Creating a VI and Sampling Music 369

Chapter 9**Sensors** 375

- 9.1 Introduction 376
- 9.2 Position and Speed Measurement 376
 - 9.2.1 Proximity Sensors and Switches 377
 - 9.2.2 Potentiometer 379
 - 9.2.3 Linear Variable Differential Transformer 380
 - 9.2.4 Digital Optical Encoder 383
- 9.3 Stress and Strain Measurement 391
 - 9.3.1 Electrical Resistance Strain Gage 392
 - 9.3.2 Measuring Resistance Changes with a Wheatstone Bridge 396
 - 9.3.3 Measuring Different States of Stress with Strain Gages 400
 - 9.3.4 Force Measurement with Load Cells 405
- 9.4 Temperature Measurement 407
 - 9.4.1 Liquid-in-Glass Thermometer 408
 - 9.4.2 Bimetallic Strip 408
 - 9.4.3 Electrical Resistance Thermometer 408
 - 9.4.4 Thermocouple 409
- 9.5 Vibration and Acceleration Measurement 414
 - 9.5.1 Piezoelectric Accelerometer 421
- 9.6 Pressure and Flow Measurement 425
- 9.7 Semiconductor Sensors and Microelectromechanical Devices 425

Chapter 10**Actuators** 431

- 10.1 Introduction 432
- 10.2 Electromagnetic Principles 432
- 10.3 Solenoids and Relays 433
- 10.4 Electric Motors 435
- 10.5 DC Motors 441
 - 10.5.1 DC Motor Electrical Equations 444

10.5.2	<i>Permanent Magnet DC Motor Dynamic Equations</i>	445
10.5.3	<i>Electronic Control of a Permanent Magnet DC Motor</i>	447
10.6	Stepper Motors	453
10.6.1	<i>Stepper Motor Drive Circuits</i>	460
10.7	Selecting a Motor	463
10.8	Hydraulics	468
10.8.1	<i>Hydraulic Valves</i>	470
10.8.2	<i>Hydraulic Actuators</i>	473
10.9	Pneumatics	474
<u>Chapter 11</u>		
Mechatronic Systems—Control Architectures and Case Studies 478		
11.1	Introduction	479
11.2	Control Architectures	479
11.2.1	<i>Analog Circuits</i>	479
11.2.2	<i>Digital Circuits</i>	480
11.2.3	<i>Programmable Logic Controller</i>	480
11.2.4	<i>Microcontrollers and DSPs</i>	482
11.2.5	<i>Single-Board Computer</i>	483
11.2.6	<i>Personal Computer</i>	483
11.3	Introduction to Control Theory	483
11.3.1	<i>Armature-Controlled DC Motor</i>	484
11.3.2	<i>Open-Loop Response</i>	486
11.3.3	<i>Feedback Control of a DC Motor</i>	487
11.3.4	<i>Controller Empirical Design</i>	491
11.3.5	<i>Controller Implementation</i>	492
11.3.6	<i>Conclusion</i>	493
11.4	Case Study 1—Myoelectrically Controlled Robotic Arm	494
11.5	Case Study 2—Mechatronic Design of a Coin Counter	507
11.6	Case Study 3—Mechatronic Design of a Robotic Walking Machine	516
11.7	List of Various Mechatronic Systems	521
<u>Appendix A</u>		
Measurement Fundamentals 523		
A.1	Systems of Units	523
A.1.1	<i>Three Classes of SI Units</i>	525
A.1.2	<i>Conversion Factors</i>	527
A.2	Significant Figures	528
A.3	Statistics	530
A.4	Error Analysis	533
A.4.1	<i>Rules for Estimating Errors</i>	534
<u>Appendix B</u>		
Physical Principles 536		
<u>Appendix C</u>		
Mechanics of Materials 541		
C.1	Stress and Strain Relations	541
Index		545