

9. For a resistance we can calculate the power as

$$P = I^2 R$$

$$P = (2.0 \text{ A})^2 (80 \ \Omega) = (4.0)(80) \text{ W}$$

$$P = 320 \text{ W}$$