

# CONTENTS

## Lists ix

- Figures ix
- Tables xv
- Class Discussion Items xvi
- Examples xviii
- Design Examples xix
- Threaded Design Examples xx

## Preface xxi

### Chapter 1

#### Introduction 1

- 1.1 Mechatronics 1
- 1.2 Measurement Systems 4
- 1.3 Threaded Design Examples 5

### Chapter 2

#### Electric Circuits and Components 12

- 2.1 Introduction 13
- 2.2 Basic Electrical Elements 15
  - 2.2.1 Resistor 15
  - 2.2.2 Capacitor 20
  - 2.2.3 Inductor 21
- 2.3 Kirchhoff's Laws 22
  - 2.3.1 Series Resistance Circuit 24
  - 2.3.2 Parallel Resistance Circuit 26
- 2.4 Voltage and Current Sources and Meters 29
- 2.5 Thevenin and Norton Equivalent Circuits 34
- 2.6 Alternating Current Circuit Analysis 36
- 2.7 Power in Electrical Circuits 42
- 2.8 Transformer 43

- 2.9 Impedance Matching 45
- 2.10 Grounding and Electrical Interference 47
  - 2.10.1 Electrical Safety 49

### Chapter 3

#### Semiconductor Electronics 58

- 3.1 Introduction 59
- 3.2 Semiconductor Physics as the Basis for Understanding Electronic Devices 59
- 3.3 Junction Diode 60
  - 3.3.1 Zener Diode 65
  - 3.3.2 Voltage Regulators 70
  - 3.3.3 Optoelectronic Diodes 71
  - 3.3.4 Analysis of Diode Circuits 73
- 3.4 Bipolar Junction Transistor 75
  - 3.4.1 Bipolar Transistor Physics 75
  - 3.4.2 Common Emitter Transistor Circuit 77
  - 3.4.3 Bipolar Transistor Switch 79
  - 3.4.4 Bipolar Transistor Packages 81
  - 3.4.5 Darlington Transistor 82
  - 3.4.6 Phototransistor and Optoisolator 82
- 3.5 Field-Effect Transistors 84
  - 3.5.1 Behavior of Field-Effect Transistors 85
  - 3.5.2 Symbols Representing Field-Effect Transistors 87
  - 3.5.3 Applications of MOSFETs 88

### Chapter 4

#### System Response 98

- 4.1 System Response 99
- 4.2 Amplitude Linearity 100
- 4.3 Fourier Series Representation of Signals 101
- 4.4 Bandwidth and Frequency Response 105

- 4.5 Phase Linearity 110
- 4.6 Distortion of Signals 111
- 4.7 Dynamic Characteristics of Systems 113
- 4.8 Zero-Order System 113
- 4.9 First-Order System 115
  - 4.9.1 Experimental Testing of a First-Order System 117
- 4.10 Second-Order System 118
  - 4.10.1 Step Response of a Second-Order System 122
  - 4.10.2 Frequency Response of a System 124
- 4.11 System Modeling and Analogies 132

## Chapter 5

### **Analog Signal Processing Using Operational Amplifiers** 143

- 5.1 Introduction 144
- 5.2 Amplifiers 144
- 5.3 Operational Amplifiers 145
- 5.4 Ideal Model for the Operational Amplifier 146
- 5.5 Inverting Amplifier 149
- 5.6 Noninverting Amplifier 151
- 5.7 Summer 154
- 5.8 Difference Amplifier 154
- 5.9 Instrumentation Amplifier 157
- 5.10 Integrator 159
- 5.11 Differentiator 160
- 5.12 Sample and Hold Circuit 161
- 5.13 Comparator 162
- 5.14 The Real Op Amp 163
  - 5.14.1 Important Parameters from Op Amp Data Sheets 164

## Chapter 6

### **Digital Circuits** 180

- 6.1 Introduction 181
- 6.2 Digital Representations 182
- 6.3 Combinational Logic and Logic Classes 185
- 6.4 Timing Diagrams 188

- 6.5 Boolean Algebra 189
- 6.6 Design of Logic Networks 191
  - 6.6.1 Define the Problem in Words 191
  - 6.6.2 Write Quasi-Logic Statements 192
  - 6.6.3 Write the Boolean Expression 192
  - 6.6.4 AND Realization 193
  - 6.6.5 Draw the Circuit Diagram 193
- 6.7 Finding a Boolean Expression Given a Truth Table 194
- 6.8 Sequential Logic 196
- 6.9 Flip-Flops 197
  - 6.9.1 Triggering of Flip-Flops 198
  - 6.9.2 Asynchronous Inputs 200
  - 6.9.3 D Flip-Flop 201
  - 6.9.4 JK Flip-Flop 202
- 6.10 Applications of Flip-Flops 204
  - 6.10.1 Switch Debouncing 204
  - 6.10.2 Data Register 206
  - 6.10.3 Binary Counter and Frequency Divider 206
  - 6.10.4 Serial and Parallel Interfaces 206
- 6.11 TTL and CMOS Integrated Circuits 208
  - 6.11.1 Using Manufacturer IC Data Sheets 210
  - 6.11.2 Digital IC Output Configurations 212
  - 6.11.3 Interfacing TTL and CMOS Devices 214
- 6.12 Special Purpose Digital Integrated Circuits 217
  - 6.12.1 Decade Counter 217
  - 6.12.2 Schmitt Trigger 221
  - 6.12.3 555 Timer 222
- 6.13 Integrated Circuit System Design 224
  - 6.13.1 IEEE Standard Digital Symbols 228

## Chapter 7

### **Microcontroller Programming and Interfacing** 238

- 7.1 Microprocessors and Microcomputers 239
- 7.2 Microcontrollers 241
- 7.3 The PIC16F84 Microcontroller 244
- 7.4 Programming a PIC 248

<b>7.5</b>	PicBasic Pro	254			
	7.5.1 PicBasic Pro Programming Fundamentals	254			
	7.5.2 PicBasic Pro Programming Examples	262			
<b>7.6</b>	Using Interrupts	273			
<b>7.7</b>	Interfacing Common PIC Peripherals	277			
	7.7.1 Numeric Keypad	277			
	7.7.2 LCD Display	280			
<b>7.8</b>	Interfacing to the PIC	285			
	7.8.1 Digital Input to the PIC	287			
	7.8.2 Digital Output from the PIC	287			
<b>7.9</b>	Method to Design a Microcontroller-Based System	289			
<u>Chapter 8</u>					
<b>Data Acquisition</b> 317					
<b>8.1</b>	Introduction	318			
<b>8.2</b>	Quantizing Theory	321			
<b>8.3</b>	Analog-to-Digital Conversion	323			
	8.3.1 Introduction	323			
	8.3.2 Analog-to-Digital Converters	327			
<b>8.4</b>	Digital-to-Analog Conversion	329			
<b>8.5</b>	Virtual Instrumentation, Data Acquisition, and Control	334			
<u>Chapter 9</u>					
<b>Sensors</b> 338					
<b>9.1</b>	Introduction	339			
<b>9.2</b>	Position and Speed Measurement	339			
	9.2.1 Proximity Sensors and Switches	340			
	9.2.2 Potentiometer	342			
	9.2.3 Linear Variable Differential Transformer	342			
	9.2.4 Digital Optical Encoder	346			
<b>9.3</b>	Stress and Strain Measurement	354			
	9.3.1 Electrical Resistance Strain Gage	354			
	9.3.2 Measuring Resistance Changes with a Wheatstone Bridge	358			
	9.3.3 Measuring Different States of Stress with Strain Gages	362			
	9.3.4 Force Measurement with Load Cells	367			
<b>9.4</b>	Temperature Measurement	370			
	9.4.1 Liquid-in-Glass Thermometer	370			
	9.4.2 Bimetallic Strip	371			
	9.4.3 Electrical Resistance Thermometer	371			
	9.4.4 Thermocouple	372			
<b>9.5</b>	Vibration and Acceleration Measurement	379			
	9.5.1 Piezoelectric Accelerometer	384			
<b>9.6</b>	Pressure and Flow Measurement	387			
<b>9.7</b>	Semiconductor Sensors and Microelectromechanical Devices	387			
<u>Chapter 10</u>					
<b>Actuators</b> 392					
<b>10.1</b>	Introduction	393			
<b>10.2</b>	Electromagnetic Principles	393			
<b>10.3</b>	Solenoids and Relays	394			
<b>10.4</b>	Electric Motors	396			
<b>10.5</b>	DC Motors	402			
	10.5.1 DC Motor Electrical Equations	405			
	10.5.2 Permanent Magnet DC Motor Dynamic Equations	405			
	10.5.3 Electronic Control of a Permanent Magnet DC Motor	407			
<b>10.6</b>	Stepper Motors	413			
	10.6.1 Stepper Motor Drive Circuits	418			
<b>10.7</b>	Selecting a Motor	422			
<b>10.8</b>	Hydraulics	426			
	10.8.1 Hydraulic Valves	428			
	10.8.2 Hydraulic Actuators	431			
<b>10.9</b>	Pneumatics	432			
<u>Chapter 11</u>					
<b>Mechatronic Systems—Control Architectures and Case Studies</b> 436					
<b>11.1</b>	Introduction	437			
<b>11.2</b>	Control Architectures	437			
	11.2.1 Analog Circuits	437			

11.2.2	<i>Digital Circuits</i>	438
11.2.3	<i>Programmable Logic Controller</i>	438
11.2.4	<i>Microcontrollers and DSPs</i>	438
11.2.5	<i>Single-Board Computer</i>	439
11.2.6	<i>Personal Computer</i>	439
<b>11.3</b>	<b>Introduction to Control Theory</b>	439
11.3.1	<i>Armature-Controlled DC Motor</i>	440
11.3.2	<i>Open-Loop Response</i>	442
11.3.3	<i>Feedback Control of a DC Motor</i>	443
11.3.4	<i>Controller Empirical Design</i>	446
11.3.5	<i>Controller Implementation</i>	448
11.3.6	<i>Conclusion</i>	449
<b>11.4</b>	<b>Case Study 1—Myoelectrically Controlled Robotic Arm</b>	449
<b>11.5</b>	<b>Case Study 2—Mechatronic Design of a Coin Counter</b>	462
<b>11.6</b>	<b>Case Study 3—Mechatronic Design of a Robotic Walking Machine</b>	471
<b>11.7</b>	<b>List of Various Mechatronic Systems</b>	477
<u>Appendix A</u>		
<b>Measurement Fundamentals</b>		479
<b>A.1</b>	<b>Systems of Units</b>	479
A.1.1	<i>Three Classes of SI Units</i>	481
A.1.2	<i>Conversion Factors</i>	483
<b>A.2</b>	<b>Significant Figures</b>	484
<b>A.3</b>	<b>Statistics</b>	486
<b>A.4</b>	<b>Error Analysis</b>	489
A.4.1	<i>Rules for Estimating Errors</i>	489
<u>Appendix B</u>		
<b>Physical Principles</b>		492
<u>Appendix C</u>		
<b>Mechanics of Materials</b>		497
<b>C.1</b>	<b>Stress and Strain Relations</b>	497
<b>Index</b>		501